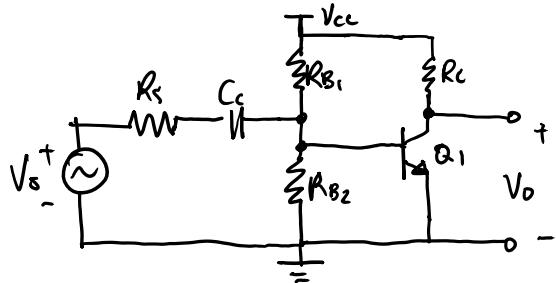


Circuit of Interest

September 7, 2017 3:29 PM


Consider common-emitter amplifier:



Where:

- V_s is source voltage, R_s is the source's internal resistance
- C_c is the coupling capacitor

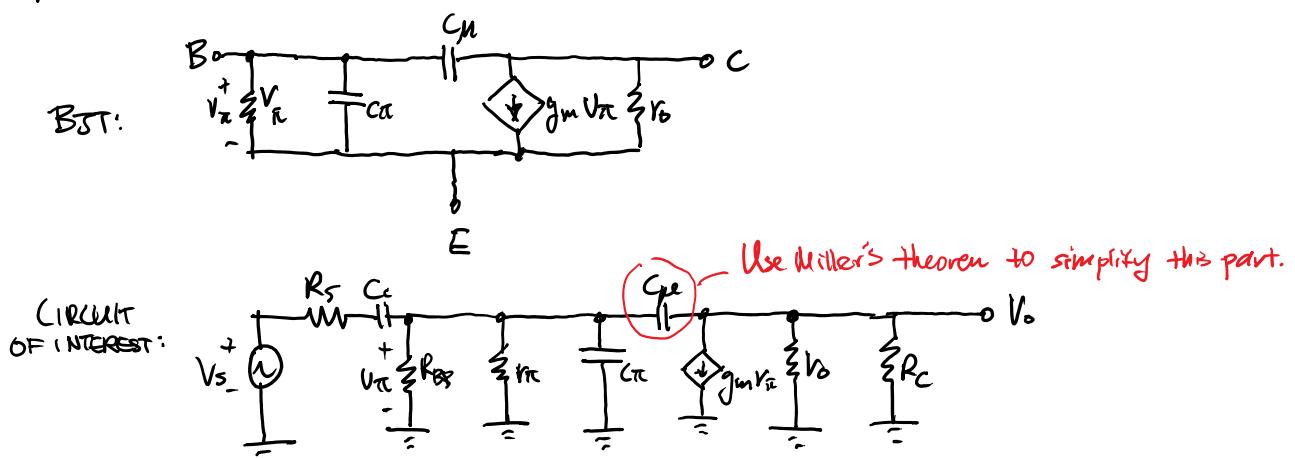
Using Small signal model, we represent the circuit using the hybrid π model



Thevenin, Norton, and Miller

September 23, 2017 11:06 PM


Thevenin:

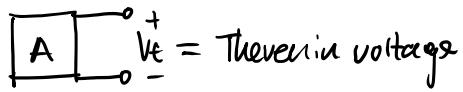

$$\boxed{A} \quad \text{V}_T = \text{Thevenin voltage}$$

$$\boxed{A} \quad \text{V}_T \quad Z_T \text{ (Thevenin impedance)} = \frac{\text{V}_T}{\text{I}_T}$$

Norton

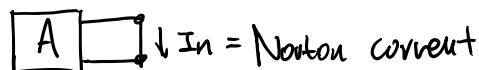


$$\boxed{A} \quad \text{I}_N = \text{Norton current}$$

$$\boxed{A} \quad \text{V}_T \quad Y_N \text{ (Norton admittance)} = \frac{\text{I}_T}{\text{V}_T}$$


NEW!

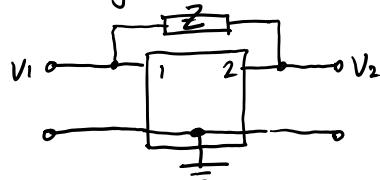Milner: (For given network where $V_2 = k V_1$):



$$\downarrow \quad Z_1 = Z \left(\frac{1}{1-k} \right)$$


$$Z_2 = Z \left(\frac{k}{1-k} \right)$$

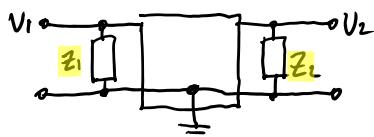

Circuit of Interest Simplified

September 23, 2017 11:16 PM


We left the BJT circuit of interest as:

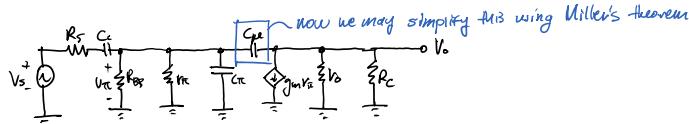

First, we can simplify the RHS:

$$V_T - \underbrace{(R_o // R_L)(-g_m V_r)}_{Z_m}$$
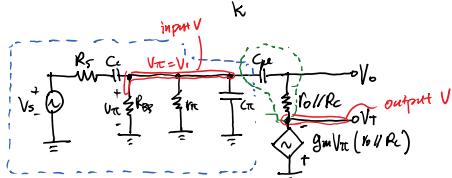
$$\text{Input} \rightarrow V_T - \underbrace{g_m(r_o // R_L)}_k V_r \leftarrow \text{Output}$$



Now let's split C_M into the **input** side and the **output** side.

Recall that: for $V_L = k V_i$, where $V_i = V_r$, $V_L = V_T$, $Z = Z_M + (r_o // R_L)$, $k = g_m r_o // R_L$

$$Z_1 = \frac{1}{(1-k)}, \quad Z_2 = \frac{k}{(1-k)}$$

INPUT

$$\begin{aligned} & V_s \xrightarrow{\text{V}_r} \xrightarrow{\text{V}_T} \xrightarrow{\text{V}_i} \xrightarrow{\text{V}_r} \xrightarrow{\text{V}_T} \xrightarrow{\text{V}_o} \\ & Z_1 = \left[Z_M + (r_o // R_L) \right] \left[\frac{1}{1 + g_m(r_o // R_L)} \right] \\ & Z_1 = \frac{1}{\frac{1}{j\omega C_M} + \frac{r_o // R_L}{1 + g_m(r_o // R_L)}} \\ & Z_1 = \frac{1}{\frac{j\omega C_M}{1 + g_m(r_o // R_L)} + \frac{r_o // R_L}{1 + g_m(r_o // R_L)}} \\ & Z_1 = \frac{1}{j\omega C_M (1 + g_m(r_o // R_L))} + \frac{r_o // R_L}{1 + g_m(r_o // R_L)} \end{aligned}$$

If $\frac{1}{j\omega C_M} \gg r_o // R_L$, and $g_m(r_o // R_L) \gg 1$, then we can further simplify:

$$\xrightarrow{\text{V}_r} \xrightarrow{\text{G}_m g_m (r_o // R_L)}$$

$$\begin{aligned} & V_s \xrightarrow{\text{V}_r} \xrightarrow{\text{V}_T} \xrightarrow{\text{V}_i} \xrightarrow{\text{V}_r} \xrightarrow{\text{V}_T} \xrightarrow{\text{V}_o} \\ & \text{G}_m g_m (r_o // R_L) \end{aligned}$$

So we essentially have 2 simple circuits

$$\begin{aligned} & V_s \xrightarrow{\text{V}_r} \xrightarrow{\text{R}_1} \xrightarrow{\text{C}_1} \xrightarrow{\text{V}_o} \\ & V_s \xrightarrow{\text{V}_r} \xrightarrow{\text{R}_2} \xrightarrow{\text{C}_2} \xrightarrow{\text{V}_o} \end{aligned}$$

OUTPUT

$$\begin{aligned} & V_o \xrightarrow{\text{C}_M} \xrightarrow{\text{V}_o} \\ & Z_2 = \left(\frac{1}{j\omega C_M} + r_o // R_L \right) \left[\frac{-g_m(r_o // R_L)}{1 + g_m(r_o // R_L)} \right] \\ & Z_2 = \frac{-g_m(r_o // R_L)}{j\omega C_M (1 + g_m(r_o // R_L))} + \frac{-g_m(r_o // R_L)^2}{1 + g_m(r_o // R_L)} \\ & Z_2 = \frac{-1}{j\omega C_M \left(\frac{1}{1 + g_m(r_o // R_L)} + 1 \right)} + \frac{-(r_o // R_L)^2}{\left(\frac{1}{1 + g_m(r_o // R_L)} + 1 \right)} \\ & \text{new capacitance} \end{aligned}$$

$$\begin{aligned} & V_x \xrightarrow{\text{V}_r} \xrightarrow{\text{R}_o} \xrightarrow{\text{C}_M (1 + g_m(r_o // R_L))^{-1}} \xrightarrow{\text{V}_o} \\ & \text{G}_m (r_o // R_L) V_r \end{aligned}$$

Similar to the input we can approximate given $g_m(r_o // R_L) \gg 1$

$$\begin{aligned} & V_x \xrightarrow{\text{V}_r} \xrightarrow{\text{R}_o} \xrightarrow{\text{C}_M} \xrightarrow{\text{V}_o} \\ & -g_m(r_o // R_L) V_r \end{aligned}$$

As far as output is concerned, this can be treated as an independent source.

Laplace Domain

September 24, 2017 3:08 PM

$$\mathcal{L}\{f(t)\} = \int_0^\infty f(t) e^{-st} dt$$

$$\mathcal{L}\{Kf(t)\} = K \mathcal{L}\{f(t)\}$$

$$\mathcal{L}\{f_1(t) \pm f_2(t)\} = F_1(s) \pm F_2(s)$$

$$\mathcal{L}\{Ke^{\alpha t}\} = \frac{K}{s-\alpha}$$

$$\mathcal{L}\left\{\frac{df(t)}{dt}\right\} = sF(s) - f(0^-)$$

$$\mathcal{L}\left\{\frac{d^2f(t)}{dt^2}\right\} = s^2F(s) - sf(0^-) - \frac{df(0^-)}{dt}$$

$$\mathcal{L}\left\{\int_0^t f(t) dt\right\} = \frac{F(s)}{s}$$

$$\mathcal{L}\{f_1(t) * f_2(t)\} = F_1(s)F_2(s)$$

$$\mathcal{L}\{e^{\alpha t} f(t)\} = F(s-\alpha)$$

$$\mathcal{L}\left\{\frac{Kt^{n-1}e^{\alpha t}}{(n-1)!}\right\} = \frac{K}{(s-\alpha)^n}$$

$$\mathcal{L}\{\sin(\omega t)\} = \frac{\omega}{s^2 + \omega^2}$$

$$s(\text{complex frequency}) = \sigma + j\omega$$

\uparrow
neper (rate at which func. grows/decays)

Ex. Given transfer function $T(s) = \frac{1000s}{(s+10)(s+100)}$, and input $v_i(t) = u(t)\sin(\omega t)$

$$V_o(s) = T(s) V_i(s)$$

$$= \underbrace{\left(\frac{s}{s+10}\right)}_{\substack{\text{low freq response} \\ (\text{high pass filter})}} \cdot \underbrace{\left(\frac{1000}{s+100}\right)}_{\substack{\text{high freq response} \\ (\text{lowpass filter})}}$$

$$= \frac{10000s}{(s+10)(s+100)(s^2+100)}$$

Setting $s = -10$, mult by $(s+10)$:

$$\rightarrow \frac{10000(-10)}{(10-1000)(200)} = -\frac{50}{99} = A$$

Setting $s = -1000$: mult $(s+1000)$

$$\rightarrow \frac{100000(-1000)}{(10-1000)(1000000+100)} = \frac{100000}{9900199} = B$$


⋮

$$= \underbrace{\frac{10000}{9900199} \left(\frac{1}{s+1000}\right)}_{\substack{\text{decaying exponentials}}} - \underbrace{\frac{50}{99} \left(\frac{1}{s+10}\right)}_{\substack{\text{sinusoidal}}} + \underbrace{\frac{4950}{10001} \left(\frac{s}{s^2+100}\right)}_{\substack{\text{sinusoidal}}} + \underbrace{\frac{5050}{10001} \left(\frac{1}{s^2+100}\right)}_{\substack{\text{sinusoidal}}}$$


Bode Plots

September 24, 2017 3:34 PM

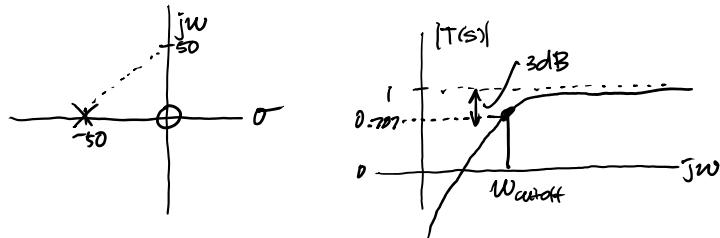
Ex. $T(s) = \frac{s}{s+10}$ (zero at zero)
(pole at -10)




Ex. $T(s) = \frac{1000}{(s+10)(s+100)}$

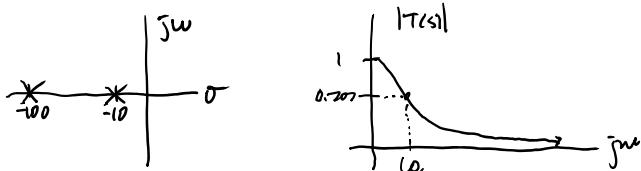

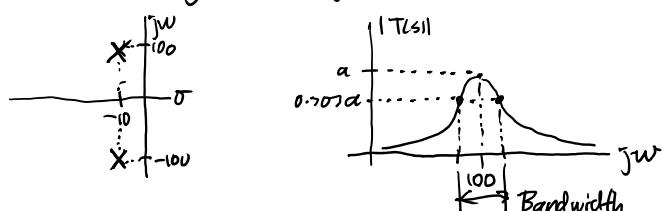
Ex. $T(s) = \frac{s}{(s+10+j100)(s+10-j100)}$



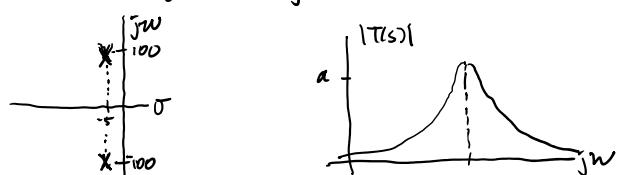Ex. $T(s) = \frac{s}{(s+5+j100)(s+5-j100)}$



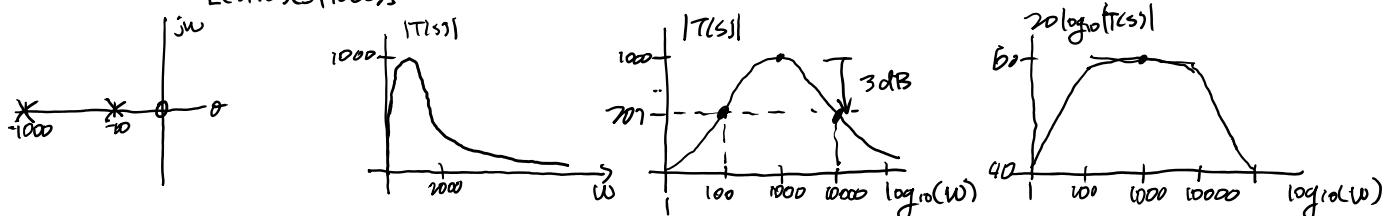Ex. $T(s) = (1000) \left[\frac{1000s}{(s+10)(s+100)} \right]$



For any transfer function $T(s)$, if we want to bode plot for positive jw axis (evaluate $s=0+jw$), we can write:

$$T(s) = T(jw) = M(w) e^{j\phi(w)}$$

magnitude of the transfer function phase of the transfer function

$$\ln |T(jw)| = \ln |M(w)| + j\phi(w)$$

$$20 \log_{10} |T(jw)| = 20 \log |M(w)|$$

Since transfer function takes the form of polynomials / polynomials,
we can simplify as:

$$\begin{aligned}
 T(s) &= K \frac{(s+w_{z_1})(s+w_{z_2})\dots}{(s+w_{p_1})(s+w_{p_2})\dots} \\
 &= K \frac{(jw+jw_{z_1})(jw+jw_{z_2})\dots}{(jw+jw_{p_1})(jw+jw_{p_2})\dots} \\
 &= K \frac{M_{z_1}(w)e^{j\arctan(\frac{w}{w_{z_1}})} M_{z_2}(w)e^{j\arctan(\frac{w}{w_{z_2}})}\dots}{M_{p_1}(w)e^{j\arctan(\frac{w}{w_{p_1}})} M_{p_2}(w)e^{j\arctan(\frac{w}{w_{p_2}})}\dots} \\
 &= K \frac{M_{z_1}(w) M_{z_2}(w)\dots}{M_{p_1}(w) M_{p_2}(w)\dots} e^{j(\arctan(\frac{w}{w_{z_1}}) + \dots - \arctan(\frac{w}{w_{p_1}})\dots)}
 \end{aligned}$$

where $M_{z_i}(w) = \sqrt{w^2 + w_{z_i}^2}$

AMPLITUDE BODE PLOT:

$$20 \log_{10}|T(s)| = 20 \log_{10}(K) + 20 \log_{10}|M_{z_1}(w)| + \dots - 20 \log_{10}|M_{p_1}(w)|\dots$$

PHASE BODE PLOT:

$$\phi(w) = \underbrace{\tan^{-1}(\frac{w}{w_{z_1}}) + \dots + \tan^{-1}(\frac{w}{w_{p_1}})}_{\text{Should add up to}} \dots$$

$\begin{matrix} 0 & \pi \\ \pm 180 & \mp \pi \end{matrix} \quad K > 0 \quad K < 0$

Low Pass, Band Pass, & High Pass

September 25, 2017 10:45 AM

$$\frac{V_o}{V_i} = \frac{\left(\frac{1}{sC}\right)}{\left(\frac{1}{sC} + R\right)} \cdot \frac{\left(\frac{s}{R}\right)}{\left(\frac{s}{R}\right)}$$


$$= \frac{\left(\frac{1}{RC}\right)}{\left(\frac{1}{RC} + s\right)}$$

$$= \frac{W_p}{s + W_p}$$


$$\rightarrow W_p = \frac{1}{RC}$$

$$\rightarrow \text{circuit has a pole at } s = -W_p$$

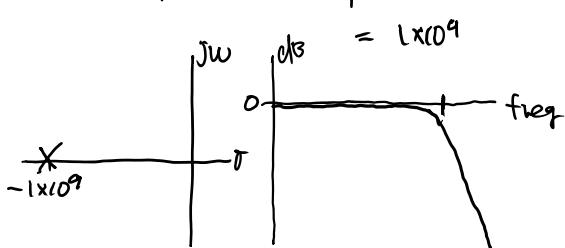ex. If $R = 1k$, $C = 1\mu F$, then $W_p = \frac{1}{1 \times 10^3 \times 10^{-6}} = 1 \times 10^9$



Given the following circuit:

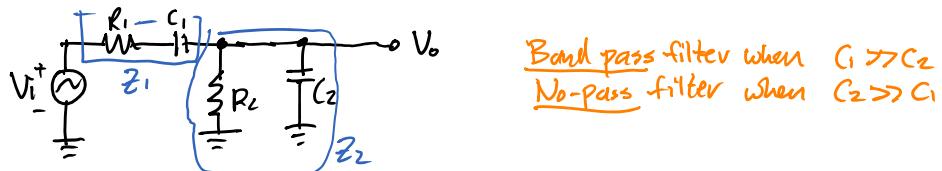

Transfer function: $\frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2}$, $Z_1 = R_1 + \frac{1}{sC_1}$, $Z_2 = R_2 // \frac{1}{sC_2}$

$$\rightarrow \frac{V_o}{V_i} = \frac{\left(\frac{1}{R_2 C_2}\right)s}{s^2 + \left(\frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} + \frac{1}{R_1 C_1}\right)s + \frac{1}{R_1 R_2 C_1 C_2}}$$

This circuit has one zero (at zero) and two poles.

Using the quadratic formula to solve the denominator into $(s + W_{p1})(s + W_{p2})$

$$\frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$\rightarrow s_{p1,2} = -\left(\frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} + \frac{1}{R_1 C_1}\right) \pm \sqrt{\left(\frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} + \frac{1}{R_1 C_1}\right)^2 - 4\left(\frac{1}{R_1 R_2 C_1 C_2}\right)}$$

We can make a few approximations:

① Since $C_1 \gg C_2$ for band pass, then $\frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} \approx \frac{1}{R_2 C_2}$

$$\approx -\frac{\left(\frac{1}{R_2 C_2} + \frac{1}{R_1 C_2}\right) \pm \sqrt{\left(\frac{1}{R_2 C_2} + \frac{1}{R_1 C_2}\right)^2 - \frac{4}{R_1 R_2 C_1 C_2}}}{2}$$

$$\left(\frac{1}{R_2 C_2} + \frac{1}{R_1 C_2}\right)^2 - \frac{4}{R_1 R_2 C_1 C_2}$$

$$\begin{aligned}
 & - \left(\frac{1}{R_2 C_2} + \frac{1}{R_1 C_2} \right)^2 - \frac{4}{R_1 R_2 C_1 C_2} \\
 & = \left(\frac{1}{R_2 C_2} \right)^2 + \frac{2}{R_1 R_2 C_2^2} + \left(\frac{1}{R_1 C_2} \right)^2 - \frac{4}{R_1 R_2 C_1 C_2}
 \end{aligned}$$

② Since $C_1 \gg C_2$, then $\frac{2}{R_1 R_2 C_2^2} \gg \frac{4}{R_1 R_2 C_1 C_2}$

$$\approx -\frac{\left(\frac{1}{R_2 C_2} + \frac{1}{R_1 C_2}\right) + \sqrt{\left(\frac{1}{R_2 C_2}\right)^2 + \frac{2}{R_1 R_2 C_2^2} + \left(\frac{1}{R_1 C_2}\right)^2}}{2}$$

$$\approx -\frac{1}{2} \left(\frac{1}{R_2 C_2} + \frac{1}{R_1 C_2} \right) + \frac{1}{2} \left(\frac{1}{R_2 C_2} + \frac{1}{R_1 C_2} \right)$$

$$S_1 \approx 0, \quad S_2 = -\left(\frac{1}{R_2 C_2} + \frac{1}{R_1 C_2}\right)$$

↓
low-freq pole is not exactly 0, so we'll have to come back to this. (w_{p1})

$$\begin{aligned}
 w_{p2} &= \frac{1}{R_2 C_2} + \frac{1}{R_1 C_2} \\
 &= \frac{1}{C_2} \left(\frac{1}{R_2} + \frac{1}{R_1} \right) \\
 &= \frac{1}{C_2} \cdot \frac{1}{R_1 // R_2} \\
 \boxed{w_{p2} = \frac{1}{C_2 (R_1 // R_2)}}
 \end{aligned}$$

Knowing w_{p2} , we can find w_{p1} :

denominator: $(s+w_{p1})(s+w_{p2}) = s^2 + (w_{p1} + w_{p2})s + w_{p1}w_{p2} = 0$.


equating w/ denominator of the transfer function ↓

$$\begin{aligned}
 s^2 + (w_{p1} + w_{p2})s + w_{p1}w_{p2} &= s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_1 C_2} + \frac{1}{R_2 C_2} \right)s + \frac{1}{R_1 R_2 C_1 C_2} \\
 w_{p1}w_{p2} &= \frac{1}{R_1 R_2 C_1 C_2} \\
 w_{p1} &= \frac{1}{w_{p2} R_1 R_2 C_1 C_2} \\
 &\approx C_2 (R_1 // R_2) \left(\frac{1}{R_1 R_2 C_2} \right) \\
 &\approx \frac{R_1 // R_2}{R_1 R_2 C_1} \\
 w_{p1} &\approx \boxed{\frac{1}{C_1 (R_1 + R_2)}}
 \end{aligned}$$


In conclusion: $w_{p1} \approx \frac{1}{C_1 (R_1 + R_2)}$

$$w_{p2} \approx \frac{1}{C_2 (R_1 // R_2)}$$

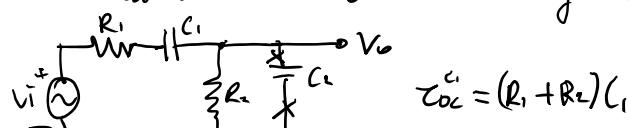Notice the w_{p1} is the $\frac{1}{T_{oc}}$, where T_{oc} is found by replacing C_2 with O.C.




$$T_{oc} = (R_1 + R_2)C_1$$

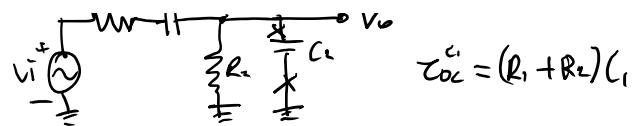

$$\tau_{oc}^{c_1} = (R_1 + R_2) C_1$$

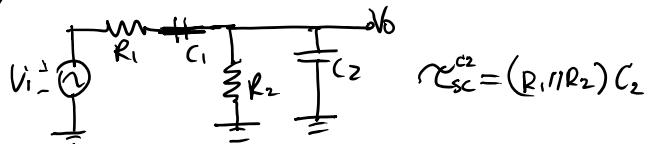Similarly, ω_{pz} is $\frac{1}{\tau_{sc}^{c_2}}$, where $\tau_{sc}^{c_2}$ is found by replacing C_1 with S.C.



$$\tau_{sc}^{c_2} = (R_1 || R_2) C_2$$

Frequency Response

September 25, 2017 5:40 PM

Recall transfer function from last part (with approx.)

$$\frac{V_o}{V_i} = \frac{\left(\frac{s}{R_1 C_2}\right)}{\left(s + \frac{1}{(R_1 + R_2)C_1}\right)\left(s + \frac{1}{(R_1 || R_2)C_2}\right)}$$

We can split into three parts: Low Freq Response
Midband,
High Freq Response

$$\rightarrow = \underbrace{\left(\frac{R_2}{R_1 + R_2}\right)}_{A_m} \underbrace{\left(\frac{s}{s + \omega_{p1}}\right)}_{F_L(s)} \underbrace{\left(\frac{\omega_{p2}}{s + \omega_{p2}}\right)}_{F_H(s)}$$


$F_L(s)$ takes the form

$$\frac{(s + \omega_{p1})(s + \omega_{p2}) \dots}{(s + \omega_{p1})(s + \omega_{p2}) \dots}$$

$F_H(s)$ takes the form

$$\frac{\omega_{p1} \omega_{p2} \dots (s + \omega_{z1H})(s + \omega_{z2H}) \dots}{\omega_{z1H} \omega_{z2H} \dots (s + \omega_{p1H})(s + \omega_{p2H}) \dots} = \frac{\left(1 + \frac{s}{\omega_{z1H}}\right)\left(1 + \frac{s}{\omega_{z2H}}\right) \dots}{\left(1 + \frac{s}{\omega_{p1H}}\right)\left(1 + \frac{s}{\omega_{p2H}}\right) \dots}$$

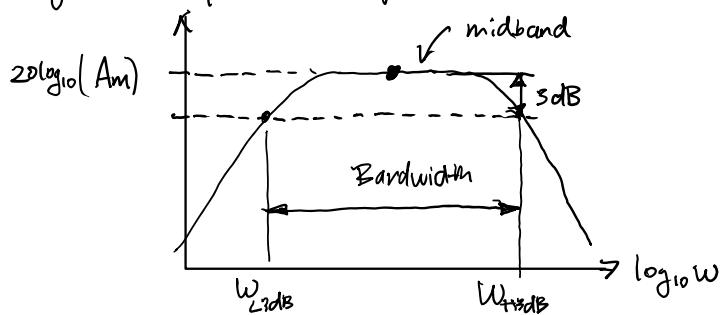Magnitude Response (of a generic bandpass filter)



Finding Cutoff Frequency

If locations of poles & zeros are known:

$$\omega_{z1dB} = \sqrt{\omega_{p1L}^2 + \omega_{p1U}^2 - 2\omega_{z1L}^2 - 2\omega_{z2L}^2 \dots}$$

$$\omega_{z2dB} = \sqrt{\left(\frac{1}{\omega_{p1H}}\right)^2 + \left(\frac{1}{\omega_{p2H}}\right)^2 - 2\left(\frac{1}{\omega_{z1H}}\right)^2 - 2\left(\frac{1}{\omega_{z2H}}\right)^2 \dots}$$

$$= \sqrt{\gamma_{p1H}^2 + \gamma_{p2H}^2 - 2\gamma_{z1H}^2 - 2\gamma_{z2H}^2 \dots}$$

If locations of poles & zeros are not known

then use method of SC and DC time constants.

Method of SL & DC Time Constants

$$F_L(s) = \frac{(s + w_{z1L})(s + w_{z2L}) \dots}{(s + w_{p1L})(s + w_{p2L}) \dots} \\ = \frac{s^N + a_1 s^{N-1} + \dots + a_N}{s^N + b_1 s^{N-1} + \dots + b_N}$$

* If one of the pole freq is > any other pole / zero freq.
Then we can make the following approximation:

$$\approx \frac{s^N}{s^N + b_1 s^{N-1}}$$

$$F_L(s) \approx \frac{s}{s + b_1}$$

where $b_1 = w_{p1L} + w_{p2L} + \dots$

$$= \frac{1}{R_{SCR}} + \frac{1}{R_{C2}} + \dots$$

$$w_{z1L} \approx b_1 = \sum_{i=1}^N \frac{1}{C_i R_i s}$$

$$F_H(s) = \frac{\left(1 + \frac{s}{w_{z1H}}\right)\left(1 + \frac{s}{w_{z2H}}\right) \dots}{\left(1 + \frac{s}{w_{p1H}}\right)\left(1 + \frac{s}{w_{p2H}}\right) \dots} \\ = \frac{1 + C_1 s + \dots + C_M s^M}{1 + d_1 s + \dots + d_M s^M}$$

* if one of the pole freq is < any other pole / zero freq.
Then we can approximate:

$$F_H(s) \approx \frac{1}{1 + d_1 s}$$

$$\text{where } d_1 = \frac{1}{w_{p1H}} + \frac{1}{w_{p2H}} + \dots \\ = \tau_{o1} + \tau_{o2} + \dots$$

$$\omega_{HedB} \approx \frac{1}{d_1} = \frac{1}{\sum_{i=1}^M C_i R_i o}$$