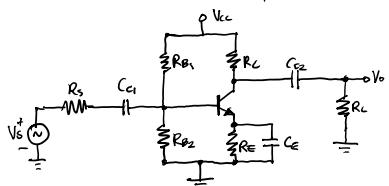



Common Emitter Amplifier

October 12, 2017 3:49 PM

Typical Common Emitter (CE) Amplifier:




DC circuit

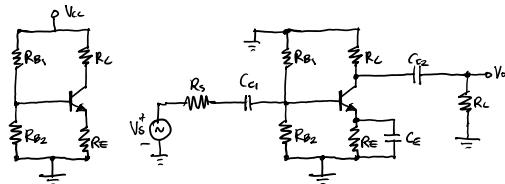


AC circuit

→ Complete Small Signal Models

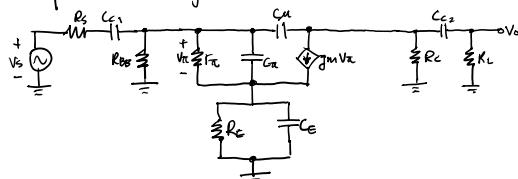


S.S. model can be split into ① Lowfrequency (LF)
② Midband (MB)
③ High frequency (HF)


① LF

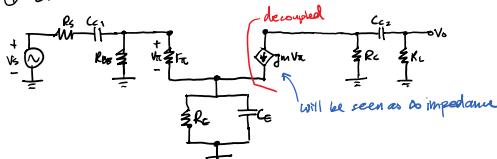

② MB

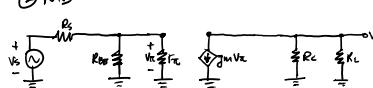

③ HF

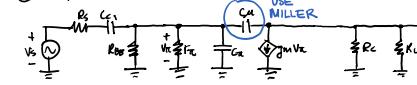

①

First, we shall find the zeroes:

C_{C1} and C_{C2} are coupling capacitors and thus have zeros at zero:

$$\omega_{LZ1} = 0, \quad \omega_{LZ2} = 0$$

Third zero is at where admittance of emitter network = 0

$$Y_E = \frac{1}{R_E} + sC_E = 0$$

$$\rightarrow s = -\frac{1}{R_E C_E}$$

Thus, we have the third pole:

$$\omega_{LZ3} = \frac{1}{R_E C_E}$$

Now we need to find the poles

The output stage B decoupled from the rest,
pole associated with C_{C2} is

$$\omega_{LP1} = (R_C + R_L) C_{C2}$$

$$\omega_{LP1} = \frac{1}{(R_C + R_L) C_{C2}}$$

For the left side, we do SCLC tests.

For C_{C1} , we short C_{C1} (R_E is neglected)

$$\omega_{SC1} = (R_S + R_{BB1} || Y_E) \cdot C_{C1}$$

For C_E , we short C_{C1} , (impedance of the base is DEMAGNIFIED by 1+ β)

This is shown by replacing C_E with a test voltage source,
calculating the test current. The impedance seen by C_E is

$$R = \frac{V_{test}}{I_{test}}$$




This is shown by replacing C_E with a test voltage source, calculating the test current. The impedance seen by C_E is

$$R = \frac{V_{test}}{I_{test}}$$

$$\tilde{Z}_{C_E} = \left(R_E \parallel \left(\frac{1}{j\omega_p} \right) (r_n + R_B \parallel R_S) \right) \cdot C_E$$

DE MAGNIFICATION

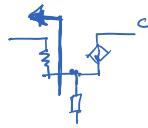


We want C_E to be an open circuit when C_{C1} conducts, hence --

OCTL test on C_{C1} (opening C_E):

$$\tilde{Z}_{C_{C1}} = [R_S + R_B \parallel (r_n + (1+\beta)R_E)] \cdot C_{C1}$$


MAGNIFICATION
(For resistances seen from the base)
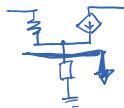
$$\text{Thus } W_{LP2} = \frac{1}{\tilde{Z}_{C_{C1}}} , \quad W_{LP3} = \frac{1}{\tilde{Z}_{C_{C2}}}$$



Finally, $F_L(s) = \underbrace{\left(\frac{s}{s + \frac{1}{\tilde{Z}_{C_{C1}}}} \right)}_{C_{C1}} \underbrace{\left(\frac{s}{s + \frac{1}{\tilde{Z}_{C_{C2}}}} \right)}_{C_{C2}} \underbrace{\left(\frac{s + \frac{1}{R_E}}{s + \frac{1}{\tilde{Z}_{C_E}}} \right)}_{C_E}$

(2) —————

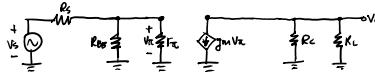


The midband gain is straightforward:

$$V_{RE} = V_s \cdot \left(\frac{R_B \parallel R_S}{R_B \parallel R_S + R_E} \right)$$

$$V_o = -g_m (R_C \parallel R_L) V_{RE}$$

$$A_{TH} = \frac{V_o}{V_s} = -g_m \left(\frac{R_B \parallel R_S}{R_B \parallel R_S + R_E} \right) (R_C \parallel R_L)$$

(2) —————

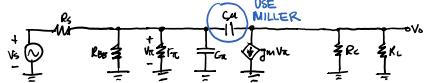

High frequency response is just like what we've done before

1. Use Miller
2. decouple output
3. Find poles (all zeroes are at ∞ (negligible)) via SCTL, OCTL tests.

(Refer to previous notes)

$$F_H(s) = \frac{(W_{HP1})}{(s + W_{HP1})} \frac{(W_{HP2})}{(s + W_{HP2})}$$