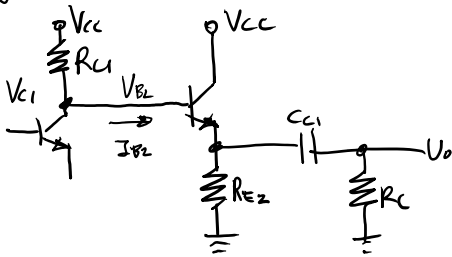


# Common Collector Amplifier

October 26, 2017 3:48 PM

- + Power Gain
- + High Input Impedence
- + Low output Impedence
- + Wide bandwidth
- + DC coupled input.

Typical CC amplifier:



$$V_{B2} = V_{C1}$$


$$I_{B2} = \frac{V_{B2} - 0.7}{(1 + \beta_2) R_{E2}} \quad (\text{mesh analysis.})$$

$$I_{C1} = \frac{V_{C1} - V_{C1}}{R_{C1}} - I_{B2}$$


Resistance seen into the base of Q2 at DC is

$$R_{in2} = \frac{V_{B2}}{I_{B2}} = \frac{V_{B2}}{V_{B2} - 0.7} (1 + \beta_2) R_{E2}$$

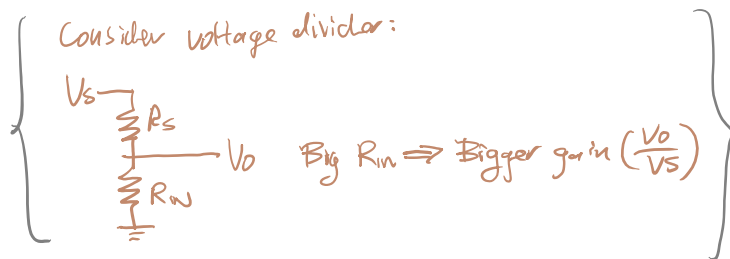For typical setup,  $R_{in2}$  will be tens of k $\Omega$ . (Large input impedance)



Small Signal Model

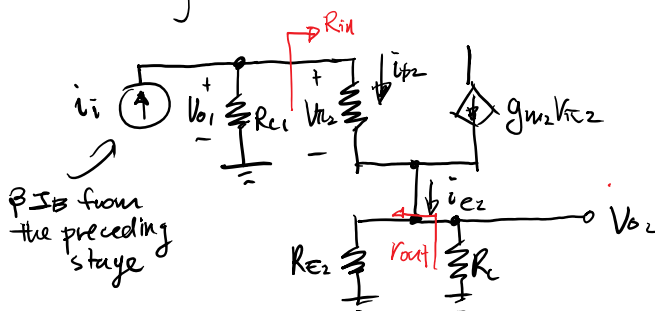

$$R_{in2} = r_{\pi 2} + (1 + \beta_2)(R_{E2} \parallel R_L)$$

$$\bar{v}_{b2} = \frac{V_{\pi 2}}{V_{o1}} = \frac{V_{o1}}{V_{o1}}$$

$$R_{in2} = r_{\pi2} + (1 + \beta_2)(R_{E2} \parallel R_L)$$

$$\bar{v}_{b2} = \frac{V_{\pi2}}{r_{\pi2}} = \frac{V_{o1}}{R_{in2}}$$

$$\begin{aligned} i_{e2} &= (1 + \beta_2) \bar{i}_{b2} \\ i_i &= \frac{V_{o1}}{R_{L1}} + \bar{i}_{b2} \end{aligned} \quad \left. \vphantom{\begin{aligned} i_{e2} &= (1 + \beta_2) \bar{i}_{b2} \\ i_i &= \frac{V_{o1}}{R_{L1}} + \bar{i}_{b2} \end{aligned}} \right\} \frac{\bar{i}_{e2}}{i_i} = \frac{(1 + \beta_2) \bar{i}_{b2}}{\left( \frac{\bar{i}_{b2} R_{in2}}{R_{L1} \parallel R_{in2}} \right)} = \frac{(1 + \beta_2) R_{L1}}{R_{L1} + r_{\pi2} + (1 + \beta_2)(R_{E2} \parallel R_L)}$$

$$\approx \frac{R_{L1}}{R_{E2} \parallel R_L}$$

(current gain)

$$\begin{aligned} &= \frac{V_{o1}}{R_{L1} \parallel R_{in2}} \\ &= \frac{\bar{i}_{b2} R_{in2}}{R_{L1} \parallel R_{in2}} \end{aligned}$$

Since  $V_{o2} = i_{e2} R_{E2} \parallel R_L$ ,


$$\frac{V_{o2}}{V_{o1}} = \frac{(1 + \beta_2)(R_{E2} \parallel R_L)}{r_{\pi2} + (1 + \beta_2)(R_{E2} \parallel R_L)}$$

$$\approx 1 \text{ (typically)}$$

$$R_{out} = R_{E2} \parallel \frac{r_{\pi2} + R_{L1}}{1 + \beta_2} \quad (\text{found by applying test source \& KVL})$$

$$\approx \frac{r_{\pi2} + R_{L1}}{1 + \beta_2}$$

High Frequency Response.

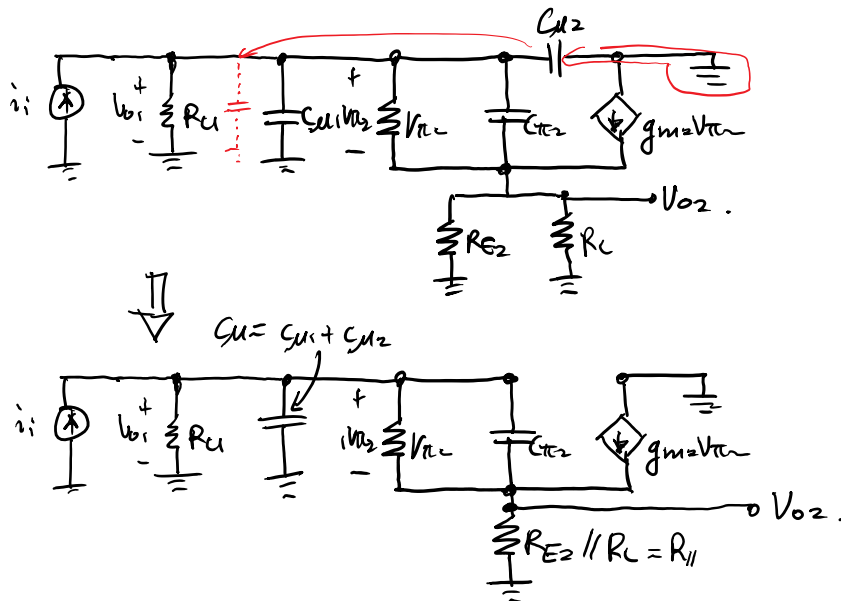


We shall do OSTC / SCTC tests:

$$\tau_{OL}^{SC} = (C_{\mu1} + C_{\mu2}) \cdot [R_{L1} \parallel (r_{\pi2} + (1 + \beta_2) R_{||})] \approx (C_{\mu1} + C_{\mu2}) R_{L1}$$

$$\tau_{SC}^{SC} = (C_{\mu1} + C_{\mu2}) (R_{L1} \parallel R_{||}) \approx (C_{\mu1} + C_{\mu2}) \cdot R_{||}$$

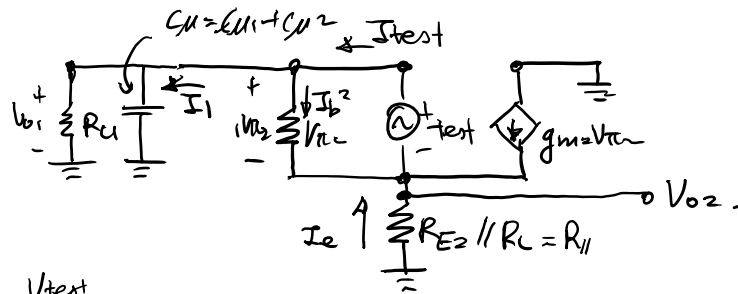For  $C_n$ , we use test source, then use OCTC/SCTC tests:



$$R_{\text{test}} = \frac{V_{\text{test}}}{I_{\text{test}}}$$

$$\begin{aligned} K_{LL}: \quad \dot{u}_{test} &= -e + \dot{u}_{b2} + g_{m2} V_a \\ &= \dot{u}_e + \dot{u}_{b2} + \beta_2 \dot{u}_2 \end{aligned}$$

KCL :  $i_{test} = i_{e2} + i_1$

$$V_{t \text{ est}} = i R_{c1} + i e R_{c1}, \text{ where } i e = i - \beta \cdot v b_2$$

$$\Rightarrow \frac{i_1}{i_{b2}} = \frac{r_{\pi 2} + \beta_2 \cdot R_{11}}{R_{L1} + R_{11}}$$

$$R_{test} = \frac{V_{test}}{I_{out}} = \frac{V_{b2} R_{n2}}{V_{b2} + i_1} = \frac{R_{n2}}{1 + \frac{i_1}{V_{b2}}} = \frac{R_{n2}}{1 + \left( \frac{R_{n2} + R_{p2} R_{n1}}{R_{c1} + R_{n1}} \right)}$$

Thus,

$$\tau_{OL}^{C_{12}} = C_{12} \cdot \left( \frac{V_{T2}}{1 + \left( \frac{V_{T2} + P_2 \cdot R_{11}}{R_L + R_{11}} \right)} \right) \approx \frac{C_{12} V_{T2}}{1 + \frac{P_2 R_{11}}{R_{11}}}$$

dominant HF poles are dictated by  $G_{\text{ext}}$ .

$$\gamma_{sc}^{G\pi_2} = G\pi_2 \left( \frac{r_{\pi_2}}{1+p_2} // R_{11} \right)$$