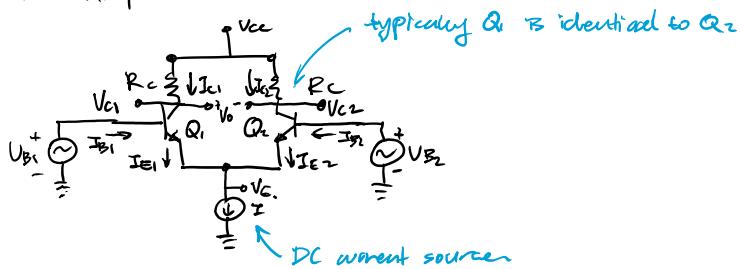


The Differential Amplifier

October 30, 2017 3:32 PM

+ doesn't need AC coupled (C_{C1}, C_{C2})

Typical Diff. Amplifier:



If $V_{B1} = V_{B2}$, then $V_{BE1} = V_{BE2}$, thus $i_{E1} = i_{E2} = I_{E1} = I_{E2} = I/2$

$$\text{Where } i_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$\text{Thus } i_{E1} = \frac{I}{2} e^{\frac{(V_B - V_E)}{V_T}}$$

$$i_{E2} = \frac{I}{2} e^{\frac{(V_B - V_E)}{V_T}}$$

Dividing by I :

$$\begin{aligned} \frac{i_{E1}}{I} &= \frac{i_{E1}}{i_{E1} + i_{E2}} \\ &= \frac{1}{1 + \frac{i_{E2}}{i_{E1}}} \\ &= \left(1 + e^{\frac{(V_{B2} - V_{B1})}{V_T}}\right)^{-1} \\ \rightarrow i_{E1} &= I \cdot \left(1 + e^{\frac{(V_{B2} - V_{B1})}{V_T}}\right)^{-1} \end{aligned}$$

$$\text{Similarly, } i_{E2} = I \cdot \left(1 + e^{\frac{(V_{B1} - V_{B2})}{V_T}}\right)^{-1}$$

Small Signal Operation requires the differential voltage (in the linear region)

$$|V_d| = |V_{B2} - V_{B1}| \ll 2V_T.$$

Using the fact $i_c = \alpha i_e$ and approximating using Taylor series,

$$\text{so } i_c \approx \alpha \frac{I}{2} \left(1 + \frac{V_d}{2V_T}\right)$$

$$\text{Similarly } i_{C2} \approx \alpha \frac{I}{2} \left(1 - \frac{V_d}{2V_T}\right)$$

Consider V_d is evenly distributed ($\pm V_d/2$ across each transistor), then


$$i_c = \alpha \frac{I}{2} \pm \frac{\alpha I}{2V_T} \frac{V_d}{2}$$

$$= I_c \pm g_m \frac{V_d}{2}$$


$$\Rightarrow g_m = \frac{\alpha I}{2V_T}$$

$$\Rightarrow i_c = g_m \frac{V_d}{2}$$


Calculating the voltage gain:

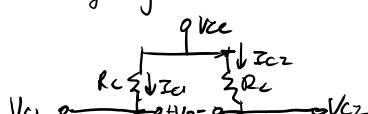

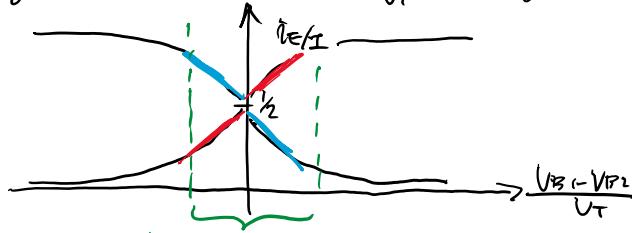Plotting i_{E1} and i_{E2} wrt $\frac{V_{B2} - V_{B1}}{V_T}$, we get:



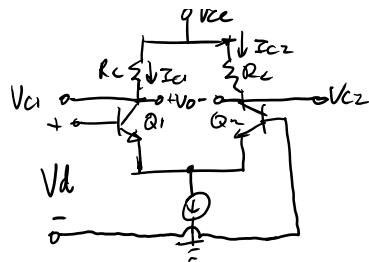the relationships are reasonably linear in this region.




Using KVL, we conclude:

$$\frac{V_o}{V_{dl}} = -g_m R_C$$

Current Mirror (Basic Current Source)

Typical current mirror setup:

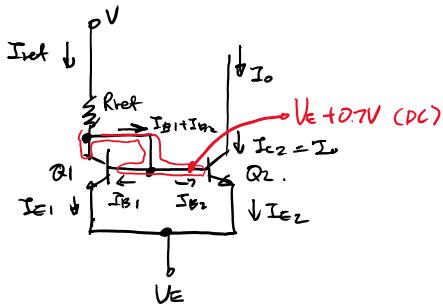

$$\text{Ohm's law: } I_{\text{ref}} = \frac{V - (V_E + V_{BE})}{R_{\text{ref}}}$$

$$KCL: I_{\text{Net}} + \cancel{I_{B1}} = I_{E1} + (\cancel{I_{B1}} + I_{B2}) \\ = I_{E1} + I_{B2}$$

$$K_{CL} = I_0 = I_{C2} = I_{E2} - I_{B2}$$

Since Q_1 and Q_2 are identical, $\sqrt{V_{B1}} = \sqrt{V_{B2}}$

Thus $I_{C1} = I_{C2}$

$$I_{ref} = I_{G1} + I_{B2}$$

$$I_{\text{ref}} - I_0 = I_{E1} + I_{B2} - (I_{E2} - I_{B2})$$

$$I_{ref} = 2I_{B2} + I_0.$$

$$S = T^2$$

$$I_{ref} = I_0 \left(1 + \frac{2}{3}\right)$$

$$\rightarrow I_0 = \frac{I_{ref}}{\left(1 + \frac{z}{B}\right)}$$