
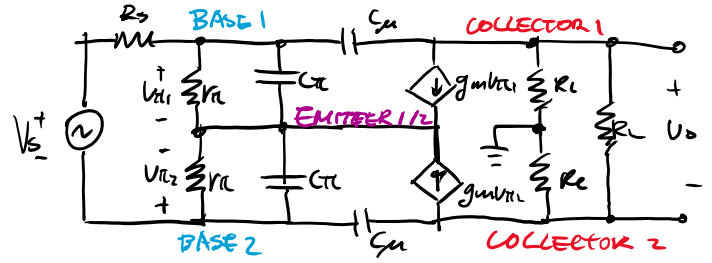


Differential Amplifier Frequency Response

October 30, 2017 4:00 PM



Small Signal Model for the D.A.:

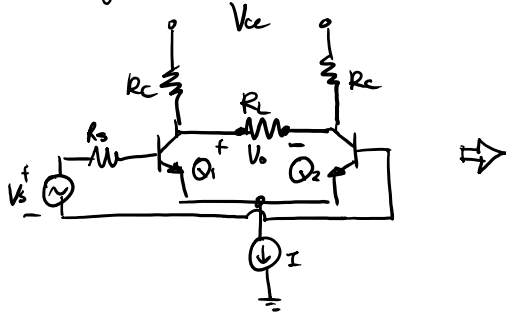

Miller gain: $k = \frac{V_o}{2V_{\pi e}} = -g_m R_c \left(\frac{R_L}{R_L + 2R_c} \right)$

So using miller to separate the capacitors, we get

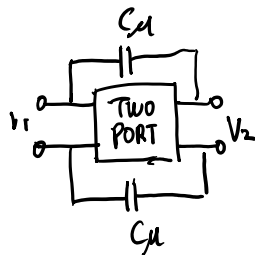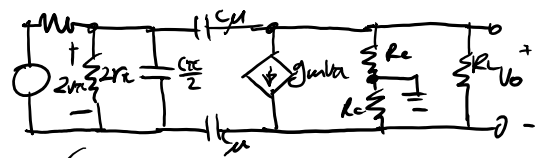
$C_{\mu 1} = C_{\mu} \cdot \frac{1}{2} (1 - k)$
 $C_{\mu 2} = C_{\mu} \cdot \frac{1}{2} (1 - \frac{1}{k})$



Miller

$$Z_1 = \frac{1}{\frac{5C_{\mu}(1-k)}{2}} \rightarrow C_{\mu 1} = \frac{C_{\mu}}{2} (1-k)$$
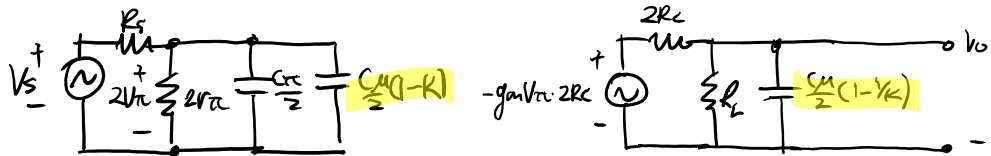
$$Z_2 = \frac{1}{\frac{5C_{\mu}}{2} (1 - \frac{1}{k})} \rightarrow C_{\mu 2} = \frac{C_{\mu}}{2} (1 - \frac{1}{k})$$



This becomes very similar to the Common Emitter amplifier except there is a factor of 2 to watch out for.

At Midband: $V_o = -g_m V_{\pi e} \cdot 2R_c \cdot \frac{R_L}{R_L + 2R_c}$, $2V_{\pi e} = V_s \cdot \frac{2r_{\pi}}{2r_{\pi} + R_s}$

$\rightarrow V_o = -g_m V_s \cdot \frac{2r_{\pi}}{2r_{\pi} + R_s} R_c \frac{R_L}{R_L + 2R_c}$

$A_{m1} = \frac{V_o}{V_s} = -g_m R_c \left(\frac{2r_{\pi}}{2r_{\pi} + R_s} \right) \left(\frac{R_L}{R_L + 2R_c} \right)$

At high frequency:

$W_{HP1} = \left[\left(\frac{C_{\pi}}{2} + \frac{C_{\mu}}{2} (1-k) \right) \cdot (R_s \parallel 2r_{\pi}) \right]^{-1}$
 $W_{HP2} = \left[\frac{C_{\mu}}{2} (1 - \frac{1}{k}) \cdot (2R_c \parallel R_L) \right]^{-1}$

$$W_{HP2} = \left[\frac{G_M}{2} (1 - \gamma_K) \cdot (2R_C \parallel R_L) \right]^{-1}$$

Since there are no coupling capacitors, low frequency is no interest for us.