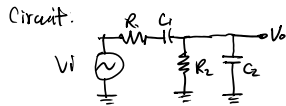


## Problem Set 2 (Again)

October 8, 2017 2:56 PM

Q1. Show that sum of the poles = sum of inverse short circuit time constants.




Short circuit test:

$$\tau_{sc}^{C_1} = C_1(R_1 + R_2)$$


C1 shorts

$$\tau_{sc}^{C_2} = C_2(R_1 \parallel R_2) = \frac{C_2}{\frac{1}{R_1} + \frac{1}{R_2}}$$
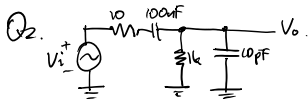
$$\begin{aligned} \text{Sum of inverse} &= \frac{1}{\tau_{sc}^{C_1}} + \frac{1}{\tau_{sc}^{C_2}} \\ &= \frac{1}{C_1(R_1 + R_2)} + \frac{(\frac{1}{R_1} + \frac{1}{R_2})}{C_2} \end{aligned}$$



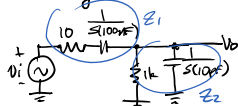a. Finding exact transfer function: b. using DC/SC test.



$$Z_1 = 10 + \frac{1}{s(100n)}$$

$$Z_2 = 1k \parallel \frac{1}{s(10p)}$$

$$\begin{aligned} \frac{V_o}{V_i} &= \frac{Z_2}{Z_1 + Z_2} \\ &= \frac{10 \times 10^{-9}}{(s + 10 \times 10^{-9})(s + 9.9k)} \end{aligned}$$

Midband:

$$\begin{aligned} \text{Midband: } \frac{V_o}{V_i} &= \frac{1000}{10 + 1000} \\ &= 0.99 \end{aligned}$$

SC test: (from low to high)

$$\tau_{sc}^{C_1} = (10 + 1000)(100nF) = 0.101ms$$

$$\omega_{p1} = 9.9k \text{ rad/s}$$

C1 shorts

$$\tau_{sc}^{C_2} = (10 \parallel 1000)(10pF) = 9.9 \times 10^{-11}s$$

$$\omega_{p2} = 10.1 \text{ Grad/s}$$

Template for T(s):


$$T(s) = A_m \cdot \frac{F_L(s)}{F_H(s)} \cdot \frac{F_H(s)}{F_L(s)}$$

$$\text{Low: } \frac{s}{s + \omega_{p1}} \quad \text{High: } \frac{\omega_{p2}}{s + \omega_{p2}}$$

Thus

$$T(s) = (0.99) \left( \frac{s}{s + 9.9k} \right) \left( \frac{10.1G}{s + 10.1G} \right)$$

Q3. Find 3dB freq.

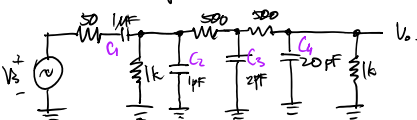

SC Test:

$$\rightarrow \tau_{sc}^{C_1} = (50 + (1000 \parallel (1000 + 500 + 1000)))(1\mu F)$$

$$= 0.717ms$$

$$\omega_{p1} = 1395 \text{ rad/s}$$

C1 shorts

$$\rightarrow \tau_{sc}^{C_2} = ((50 \parallel 1000) + 500 + 500) \parallel (1000) \cdot (20pF)$$

$$= 1.023 \times 10^{-8}s$$

$$\omega_{p2} = 97.73 \text{ Mrad/s}$$

C4 shorts

$$\rightarrow \tau_{sc}^{C_3} = ((50 \parallel 1000) + 500) \parallel 500 \cdot (2pF)$$

$$= 5.227 \times 10^{-10}s$$

$$\omega_{p3} = 1.918 \text{ Grad/s}$$

C3 shorts

$$\rightarrow \tau_{sc}^{C_4} = ((50 \parallel 1000) \parallel 500) \cdot 1\mu F$$

$$\begin{aligned} \omega_{c3dB} &= \sqrt{\omega_{p1}^2 + \omega_{p2}^2 + \dots} \\ &= \sqrt{(1395)^2} \\ &= 1395 \text{ rad/s} \end{aligned}$$

$$\begin{aligned} \tau_{HdB} &= \sqrt{\tau_{p1}^2 + \tau_{p2}^2 + \dots} \\ &= \sqrt{(1.023 \times 10^{-8})^2 + (5.227 \times 10^{-10})^2 + (4.928 \times 10^{-11})^2} \\ &= 1.024 \times 10^{-8}s \end{aligned}$$

$$\omega_{c3dB} = 97.6 \text{ Mrad/s}$$

$$\omega_{ps} = 1.919 \text{ Grad/s}$$

$C_3$  shorts

$$\rightarrow \tau_{C_3} = ((50 // 1000) // 500) \cdot 1\text{pF}$$

$$= 4.348 \times 10^{-11} \text{ s}$$

$$\omega_{ps} = 23 \text{ Grad/s}$$


Q4.  $\omega_{Lz1} = 100 \text{ rad/s}$ ,  $\omega_{Lz2} = 0 \text{ rad/s}$   
 $\omega_{Lp1} = 200 \text{ rad/s}$ ,  $\omega_{Lp2} = 50 \text{ rad/s}$

$$\omega_{Lzps} = \sqrt{\omega_{Lp1}^2 + \omega_{Lp2}^2 - 2\omega_{Lz1}\omega_{Lz2} - 2\omega_{Lz1}\omega_{Lz2}}$$

$$= \sqrt{200^2 + 50^2 - 2(100)^2 - 2(0)^2}$$

$$= \boxed{150 \text{ rad/s}}$$

Q5. Use Miller

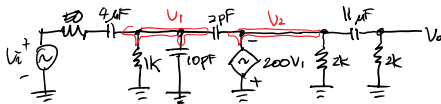


$$V_2 = -200 V_1, \text{ thus } k = -200$$

Miller:  $Z_1 = Z(\frac{1}{1-k})$ ,  $Z_2 = Z(\frac{k}{k-1})$

$$C_{M1} = C_M(1-k), C_{M2} = C_M(\frac{k-1}{k})$$

Then  $C_{M1} = 2\text{pF}(1+200)$ ,  $C_{M2} = 2\text{pF}(\frac{-200-1}{-200})$   
 $= 402\text{pF}$   $\approx 2\text{pF}$

And circuit becomes:

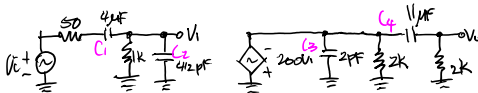

We solve midband first:

$$V_1 = \frac{1000}{1050} V_i$$

$$V_0 = -200 \left( \frac{1000}{1050} \right) V_i$$

$$A_{mid} = \frac{V_0}{V_i} = \boxed{-190.476}$$

Next, low freq response:

$$\tau_{C_1} = (50 + 1050) \cdot 4\text{pF}$$

$$= 0.0042 \text{ s}$$

$$\omega_{Lp1} = 238.1 \text{ rad/s}$$

$$\tau_{C_2} = (200)(11\text{pF})$$

$$= 0.022$$

$$\omega_{Lp2} = 45.455 \text{ rad/s}$$

Finally, high freq response:

( $C_1$  and  $C_2$  shorted)

$$\tau_{C_3} = (50 // 1k) \cdot 412\text{pF}$$

$$= 1.962 \times 10^{-8} \text{ s}$$

$$\omega_{Hps} = 50.97 \text{ Mrad/s}$$

$$\tau_{C_4} = (0)(2\text{pF})$$


$$\omega_{Hps} = \infty \text{ rad/s}$$

$$F_H(s) = \frac{50.97M}{(s + 50.97M)} \cdot \left( \frac{\omega}{s + \omega} \right)$$


$$\lim_{\omega \rightarrow \infty} \left( \frac{\omega}{s + \omega} \right) + 1 = 1$$

$$F_H(s) = \left( \frac{50.97M}{s + 50.97M} \right)$$
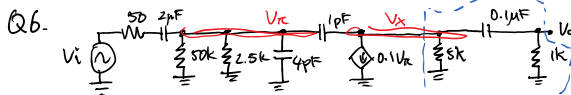
$$T(s) = -190.476 \cdot \frac{s^2}{(s + 238.1)(s + 45.5)} \cdot \frac{50.97M}{s + 50.97M}$$



Look at midband for k

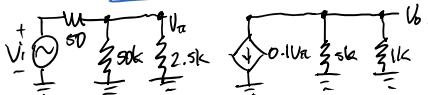

$$V_x = \frac{50k // 2.5k}{50k // 2.5k + 50} V_i$$

$$V_0 = -0.1(5k // 1k) \cdot \frac{50k // 2.5k}{50k // 2.5k + 50} V_i$$

$$\frac{V_0}{V_i} = k = \boxed{-81.619}$$

Applying Miller:

$$C_{M1} = 1\text{pF}(1-k) \quad C_{M2} = 1\text{pF}\left(\frac{k+1}{k}\right)$$


$$= 82.62\text{pF} \quad = 0.988\text{pF}$$

THEVENIN: find k

$$Z_0 = \left( \frac{1}{s \cdot 0.1\text{pF}} + 1k \right) // 5k$$

$$V_{th} = -0.1V_x \cdot Z_0$$

$$V_{th} = -0.1Z_0 V_x$$

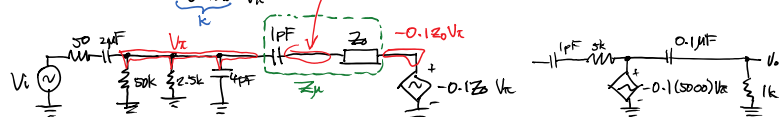


MILLER: separate LHS & RHS

$$Z_M = \frac{1}{s(1\text{pF})} + Z_0, \quad Z_0 = \left( \frac{1}{s \cdot 0.1\text{pF}} + 1k \right) // 5k$$

Applying Miller:

$$C_{\mu} = 1 \text{ pF} (1 - K) \quad C_{\mu 2} = 1 \text{ pF} \left( \frac{K+1}{K} \right)$$
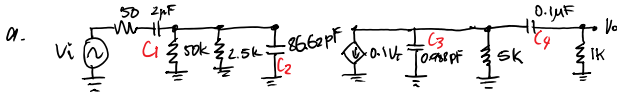
$$= 82.62 \text{ pF} \quad = 0.988 \text{ pF}$$



b. midband gain  $A_m = -81.619$

c. Find all poles.

Low freq:

$$\tau_{SC}^L = [50 + (50k \parallel 2.5k)] \cdot 2 \mu\text{F}$$

$$= 4.862 \text{ ms}$$

$$\omega_{p1} = 205.681 \text{ rad/s}$$

$$\tau_{SC}^H = (5k + 1k) (0.1 \mu\text{F})$$

$$= 0.6 \text{ ms}$$

$$\omega_{p2} = 1666.7 \text{ rad/s}$$

High freq:

$$\tau_{SC}^L = (50 \parallel 50k \parallel 2.5k) \cdot 86.62 \text{ pF}$$

$$= 4.242 \text{ ns}$$

$$\omega_{p1} = 235.702 \text{ Mrad/s}$$

$$\tau_{SC}^H = (5k \parallel 1k) \cdot 0.988 \text{ pF}$$

$$= 8.233 \times 10^{-10} \text{ s}$$

$$\omega_{p2} = 1.215 \text{ Grad/s}$$

d. transfer function:

$$T(s) = A_m \cdot F_L(s) \cdot F_H(s)$$

$$= (-81.619) \left[ \frac{s}{s + 205.681} \right] \left[ \frac{s}{s + 1666.7} \right] \left[ \frac{236 \times 10^6}{s + 236 \times 10^6} \right] \left[ \frac{1.215 \times 10^9}{s + 1.215 \times 10^9} \right]$$

3dB frequencies:

$$\omega_{3dB} = \sqrt{\omega_{p1}^2 + \omega_{p2}^2} = 1679 \text{ rad/s}$$

$$\tau_{3dB} = \sqrt{\tau_{p1}^2 + \tau_{p2}^2} = 4.321 \mu\text{s}$$

$$\omega_{H3dB} = 231.4 \text{ Mrad/s}$$