

Problem Set 3 (Again)

October 30, 2017 10:57 AM

- For the circuit shown in figure 1, use the $1/3^{\text{rd}}$ rule with $V_{CE} = V_{CC}/3$ to find R_{B1} , R_{B2} , R_C , and R_E given that $V_{CC} = 15V$ and $I_C = 2mA$.
- For the circuit shown in figure 1, use the $1/3^{\text{rd}}$ rule with $V_{CE} = V_{CC}/3$ to find R_{B1} , R_{B2} , R_C , and R_E given that $R_E = 8k\Omega$ and $V_{CC} = 12V$. (Answers: $R_{B1} = 146k\Omega$, $R_{B2} = 104k\Omega$, $R_C = 8k\Omega$, and $I_C = 0.5mA$.)
- What are g_m and r_{π} for the transistors in P1 and P2 above? (Answers: P1 $g_m = 80m\Omega^{-1}$ and $r_{\pi} = 1.25k\Omega$; P2 $g_m = 20m\Omega^{-1}$ and $r_{\pi} = 5k\Omega$.)
- Assuming that a small-signal a.c. voltage source with a 50Ω source impedance is coupled to the amplifier of P2 above via a $10\mu F$ coupling capacitor and that R_E is bypassed using a $50\mu F$ capacitor and that the hybrid-model has the following parameters: $\beta = 100$, $r_{\pi} = 2k\Omega$, and $g_m = 10mA/V$, what are A_v , ω_{L1} , and ω_{H1} ? (Answers: $A_v = -15$, $\omega_{L1} = 400\pi/s$, and $\omega_{H1} = 4.4 \times 10^4/s$.)

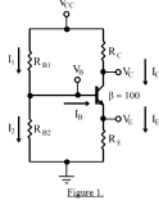


Figure 1

Q2. Second $1/3$ rule: $V_E = 1/3 V_{CC}$, $V_C = 2/3 V_{CC}$, $I_E = I_C = I_B$

Given $\rightarrow V_{CC} = 15V$, $R_E = 5k\Omega$

$V_E = 5V$, $V_C = 10V$, $V_B = 4.7V$

$I_E = \frac{V_E}{R_E} = \frac{5V}{5k\Omega} = 1mA$

$I_B = \frac{I_E}{\beta} = \frac{1mA}{100} = 10\mu A$

$I_C = \beta I_B = 1mA$


$V_C = 10V$, $R_C = \frac{V_C - V_{CE}}{I_C} = \frac{10V - 5V}{1mA} = 5k\Omega$

$I_E = \frac{I_C}{\beta} = \frac{1mA}{100} = 10\mu A$

$V_B = 4.7V$, $R_{B1} = \frac{V_{CC} - V_B}{I_B} = \frac{15V - 4.7V}{10\mu A} = 1.04k\Omega$

$I_E = I_C = 1mA$

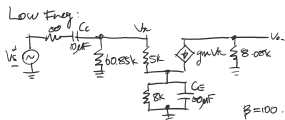$V_E = 5V$, $R_{E2} = \frac{V_E}{I_E} = \frac{5V}{1mA} = 5k\Omega$



— SC TC test: —

$\tau_{CL} = (50 + (60k\Omega // 5k\Omega)) // 10\mu F = 49ms$

$\tau_{CE} = [(50 // 60k\Omega // 5k\Omega) // 10\mu F] // 8k\Omega = 2.48ms$

— DC TC test —

$\tau_{CL} = [50 + 60k\Omega // (5k\Omega + (10\mu F // 8k\Omega))] // 10\mu F = 0.367s$

$\omega_{LP1} = 402.6 rad/s$

$\omega_{LP2} = 1.76 rad/s$

$\omega_{LP3} = 0$

$\omega_{LP4} = \frac{1}{8k\Omega // 10\mu F} = 7.5 rad/s$

$\omega_{LP5} = \frac{(1.76^2 + 402.6^2) - 2 \times 1.76 \times 402.6}{2 \times 1.76 \times 402.6} = 402.6 rad/s$

$F(s) = \frac{(s + 2.5)}{(s + 402.6)(s + 1.76)}$

Q1. First $1/3$ rule: $V_B = 1/3 V_{CC}$, $V_C = 2/3 V_{CC}$, $I_E = I_C = I_B$

$V_C = 10V$, $I_C = 2mA$

$V_E = 5V$, $V_B = 4.7V$, $V_C = 10V$

$I_C = \frac{V_C - V_{CE}}{R_C} = \frac{10V - 5V}{2.5k\Omega} = 2mA$

$I_B = \frac{I_C}{\beta} = \frac{2mA}{100} = 20\mu A$

$I_E = I_C + I_B = 2.02mA$

$R_E = \frac{V_E}{I_E} = \frac{5V}{2.02mA} = 2.47k\Omega$

$I_E = \frac{I_C}{\beta} = \frac{2.02mA}{100} = 20.2\mu A$

$V_C = 10V$, $R_{B1} = \frac{V_{CC} - V_C}{I_B} = \frac{15V - 10V}{20\mu A} = 250k\Omega$

$I_C = I_E = 2.02mA$

$V_E = 5V$, $R_{B2} = \frac{V_E}{I_E} = \frac{5V}{2.02mA} = 2.47k\Omega$

Q3. $g_m = \frac{I_C}{V_T}$, $r_{\pi} = \frac{\beta}{g_m}$


Part 1: $g_m = \frac{2mA}{25mV} = 0.080V^{-1}$

$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{0.080} = 1.25k\Omega$

Part 2: $g_m = \frac{0.5mA}{25mV} = 0.020V^{-1}$

$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{0.020} = 5k\Omega$

Q4. Small signal model:

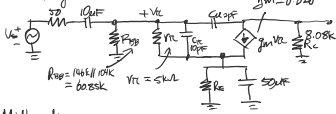

Midband:

$V_C = \frac{(60k\Omega // 5k\Omega)}{(60k\Omega // 5k\Omega) + 50} V_S = \frac{(0.080V^{-1})(5k\Omega)}{(0.080V^{-1})(5k\Omega) + 50} V_S = 0.98V_S$

$V_E = -g_m V_C (8.08k\Omega) = -(0.020)(0.98V_S)(8.08k\Omega) = -1.59V_S$

$V_O = -g_m V_C (8.08k\Omega) = -(0.020)(0.98V_S)(8.08k\Omega) = -1.59V_S$

$V_O = -1.59V_S = A_m V_S$

$A_m = -1.59$

$\tau_{HP1} = (50 // 60k\Omega // 5k\Omega) // 33.3\mu F = 1.67 \times 10^{-3}s$

$\tau_{HP2} = (8.08k\Omega) // 2\mu F = 1.61 \times 10^{-3}s$


$\tau_{HP3} = \sqrt{\tau_{HP1}^2 + \tau_{HP2}^2} = 42.95ms$

$\omega_{HP3} = \frac{1}{42.95ms} = 23.3 rad/s$

$F_H(s) = \frac{(60M)(56M)}{(s + 60M)(s + 56M)}$

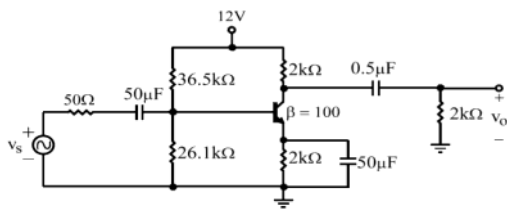5) For the circuit shown in figure 2:


- Draw the low frequency circuit, the midband circuit and the high frequency circuit and
- Derive the complete transfer function using $I_E = I_C = 2mA$, $C_{\pi} = 10pF$, and $C_{\mu} = 2pF$.



Biasing:

$V_{CC} = 12V$, $I_E \approx I_C = 2mA$, $I_B = 20\mu A$.
 $g_m = \frac{I_C}{V_T} = \frac{2mA}{25mV} = 0.080V^{-1}$.
 $r_{\pi} = \frac{\beta}{g_m} = \frac{100}{0.080} = 1.25k\Omega$.
 $V_C = 10V$, $V_E = 4V$, $V_B = 4.7V$.
 $I_E = 2.02mA$, $I_C = 2.02mA$.

Small signal:

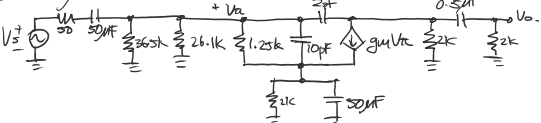

$V_C = \frac{(36.5k // 26.1k // 1.25k)}{(36.5k // 26.1k // 1.25k) + 50} V_S = 0.98V_S$

$V_E = -g_m V_C (1k) = -(0.080)(0.98V_S)(1k) = -0.078V_S$

$V_O = -g_m V_C (1k) = -(0.080)(0.98V_S)(1k) = -0.078V_S$

$V_O = -0.078V_S = A_m V_S$


$A_m = -0.078$

$\tau_{HP1} = (50 // 36.5k // 26.1k // 1.25k) // 10\mu F = 8.24 \times 10^{-3}s$

$\tau_{HP2} = (2pF)(1k) = 2 \times 10^{-9}s$

$\omega_{HP2} = \frac{1}{2 \times 10^{-9}s} = 500Mrad/s$

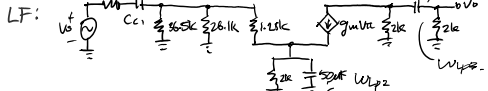$F_H(s) = \frac{(117.7M)(500M)}{(s + 117.7M)(s + 500M)}$



DC TC test (small a.c. freq)

$\tau_{CL} = 50\mu F // (50 + 36.5k // 26.1k // 1.25k + (10\mu F // 2k)) = 0.710s$

$\tau_{CE} = 50\mu F // ((36.5k // 26.1k // 1.25k) // 10\mu F) // 2k = 0.008s$

SC TC test

$\tau_{CL} = 50\mu F // ((50 // 36.5k // 26.1k) // 1.25k) // 2k = 0.639ms$


$\omega_{LP1} = 1.408 rad/s$

$\omega_{LP2} = 1619.6 rad/s$

$\omega_{LP3} = 0$

$\omega_{LP4} = 0 rad/s$

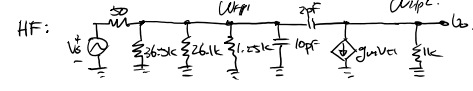$\omega_{LP5} = \frac{1}{2k // 50\mu F} = 10 rad/s$



$K = g_m (1k) = 0.08(1k) = 80$

$\rightarrow C_{\pi1} = 162pF$, $C_{\mu2} = 2pF$

$\tau_{HP1} = (10pF + 162pF) // (50 // 36.5k // 26.1k // 1.25k) = 8.24 \times 10^{-3}s$

$\omega_{HP1} = 121.3Mrad/s$

$\tau_{HP2} = (2pF)(1k) = 2 \times 10^{-9}s$

$\omega_{HP2} = 500Mrad/s$

$F_H(s) = \frac{(117.7M)(500M)}{(s + 117.7M)(s + 500M)}$

$$\omega_{Lp1} = 1.408 \text{ rad/s}$$

$$\omega_{Lp2} = 1619.6 \text{ rad/s}$$

$$\omega_{Lp3} = (4k \cdot 0.5 \mu F)^{-1} = 500 \text{ rad/s}$$

$$F_L = \left(\frac{s}{s+1.408} \right) \left(\frac{s+10}{s+1620} \right) \left(\frac{s}{s+500} \right)$$

$$\omega_{Lz1} = \omega_{Lz3} = 0 \text{ rad/s}$$

$$\omega_{Lz2} = \frac{1}{2k \cdot 50 \mu F} = 10 \text{ rad/s}$$

$$= -0.080(11k \cdot 0.959) V/s$$

$$\frac{V_o}{V_i} = \boxed{-76.681}$$

$$= 2 \times 10^{-9} s \quad \omega_{Lp2} = 520 \text{ rad/s}$$

$$F_H(s) = \left(\frac{117.7M}{s+17.7M} \right) \left(\frac{520M}{s+520M} \right)$$