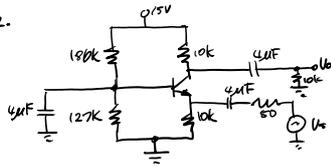



# Problem Set 4 (Again)

October 30, 2017 5:49 PM

Q2.



Biasing:

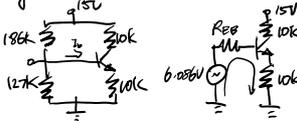

$$V_{BE} = 0.086V$$

$$R_{EB} = 75.47k$$

$$KVL: V_{BE} = i_b \cdot R_{EB} + 0.7 + (1+\beta)i_b \cdot 10k$$

$$\rightarrow i_b = \frac{V_{BE} - 0.7}{R_{EB} + (1+\beta)10k} = 4.762\mu A$$


$$i_c = \beta i_b = 0.496mA$$

$$I_E = 0.501mA$$

$$g_m = 0.01995V^{-1}$$

$$r_e = \frac{100}{g_m} = 5k\Omega$$

LF:

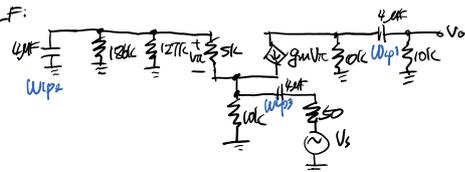

$$\omega_{LP1} = (4\mu F \cdot 20k)^{-1} = 12.5 \text{ rad/s}$$

SCTC test (loading for big freq):

$$\tau_{SC}^{(1)} = 4\mu F [180k \parallel 127k \parallel (5k + (1+\beta)(10k \parallel 150))] = 0.095s$$

$$\omega_{LP2} = 28.25 \text{ rad/s}$$

$$\tau_{SC}^{(2)} = 4\mu F [(1+\beta)(5k \parallel 10k) + 50] = 3.97 \times 10^{-4}s$$

$$\omega_{LP3} = 2517 \text{ rad/s}$$

DC test


$$\tau_{DC} = 4\mu F [180k \parallel 127k \parallel 5k + (1+\beta)10k] = 0.231s$$

$$\omega_{LP2} = 3.56 \text{ rad/s}$$

$$\omega_{LP2} = \frac{1}{4\mu F (180k \parallel 127k)} = 33 \text{ rad/s}$$

$$\omega_{LP3} = 2517 \text{ rad/s}$$

MB:

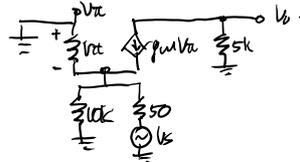


$$V_{TC} = -V_E \quad V_E = \frac{((\frac{1}{\beta})r_e \parallel 10k)}{(\frac{1}{\beta})r_e \parallel 10k + 50} V_s$$

$$V_{TC} = -0.496 V_s$$

$$V_o = -0.01985 \cdot 5k \cdot (-0.496) V_s$$

$$A_{m1} = \frac{V_o}{V_s} = 49.256 \frac{V}{V}$$

HF:

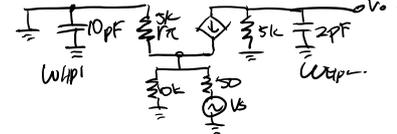

$$\tau_{HP1} = 10pF \cdot (5k + (1+\beta)(10k \parallel 50)) = 1 \times 10^{-7}s$$

$$\omega_{HP1} = 9.975M \text{ rad/s}$$


$$\tau_{HP2} = 2pF \cdot 5k = 1 \times 10^{-8}s$$

$$\omega_{HP2} = 100M \text{ rad/s}$$

$$\omega_{HBdB} = 9.75M \text{ rad/s}$$

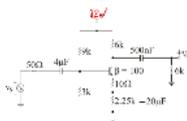3) For the circuit shown in Figure 3:

- Draw the low-frequency circuit, the midband circuit and the high-frequency circuit and
- Determine the midband gain,  $A_m$ , and  $F_{L3dB}$ .



Bias Conditions:

$$V_B \approx 3V \text{ since } I_1 \rightarrow I_B$$

$$V_E = 2.3V, I_E = \frac{2.3V}{2.2k} \approx 1mA$$


$$I_C \approx 1mA \quad I_1 = \frac{V_B - V_E}{1k} = 1mA$$

$$I_B = \frac{I_C}{\beta} = 10\mu A, I_2 = 1mA$$

$$g_m = \frac{I_C}{V_T} = \frac{1mA}{25mV} = 0.0402V^{-1}$$

$$r_e = \frac{V_T}{g_m} = \frac{100}{0.04} = 2.5k\Omega$$

MB:

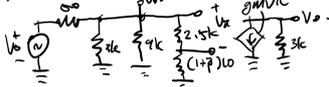


$$V_{TC} = V_o - V_E, \quad V_E = i_e \cdot 10k = i_b \cdot (1+\beta)10k$$

$$\text{Voltage divider: } V_o = \frac{3k \parallel 10k \parallel (2.5k + (1+\beta)10)}{3k \parallel 10k \parallel (2.5k + (1+\beta)10) + 50} V_s$$


$$V_o = 0.965V_s$$

$$r_{in} = \frac{V_o}{V_s}$$


Small Signal Model

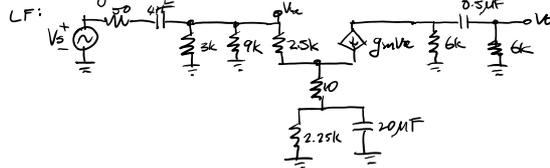

MB:

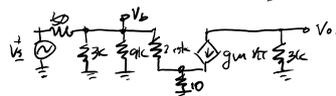

HF:

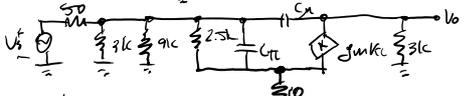

$$LF: \omega_{LP1} = \frac{1}{(6k + 6k) \cdot 0.5\mu F} = 167 \text{ rad/s}$$

DC test (want low freq)

$$\tau_{DC}^{(1)} = 4\mu F \cdot (50 + 3k \parallel 1k \parallel (2.5k + (1+\beta)(10 + 2.5k))) = 0.091s$$

$$\omega_{LP2} = 109 \text{ rad/s}$$

$$\tau_{DC}^{(2)} = \left[ \frac{1}{3k \parallel 1k} + 7.5k \right] \cdot (1+\beta) \cdot 10 + 2.5k \cdot 20\mu F = 0.002s$$

SCTC test:

$$V_b = 0.965 V_s$$

$$i_b = \frac{V_b}{2.7k + (1+p)10} = 2.749 \times 10^{-4} A$$

$$V_{rc} = 0.965 V_b - (2.749 \times 10^{-4}) V_b \cdot (1+p)(10)$$

$$V_{rc} = 0.687 V_s$$

$$V_o = -g_m V_{rc} (2k)$$

$$= -0.04 \cdot 0.687 V_s \cdot 3k$$

$$\frac{V_o}{V_b} = -82.44$$

$$= 0.0023 X$$

SCTC test:

$$\tau_{SC}^{CE} = \left[ \left( (50 + 2.5k) \cdot \left( \frac{1}{1+p} \right) + 10 \right) // 2.5k \right] \cdot 20 \mu F$$

$$= 0.694 \times 10^{-3} s$$


$$\omega_{LP3} = 1441 \text{ rad/s}$$

$$\omega_{LP1} = \omega_{LP2} = 0$$


$$\omega_{LP3} = \frac{1}{R_E \tau_{CE}} = 22.2 \text{ rad/s}$$

$$F_L(s) = \left( \frac{s}{s+1167} \right) \left( \frac{s}{s+109} \right) \left( \frac{s+22.2}{s+1441} \right)$$

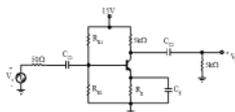4) For the circuit shown in figure 4, use the 1/3<sup>rd</sup> rule (your choice) to bias the circuit and find  $C_E$ ,  $C_{C1}$ , and  $C_{C2}$  that will put the low frequency poles at 1000/s, 100/s and 10/s. Choose the lowest cost combination of capacitors.



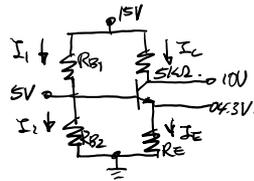Using the first 1/3 rule:  $V_B = \frac{1}{3} V_{cc}$ ,  $V_C = \frac{2}{3} V_{cc}$ ,  $I_1 = \frac{I_E}{\beta}$ ,  $\beta = 100$ .



$$V_C = 10V, V_B = 5V, V_E = 4.3V$$

$$I_E = \frac{5V}{5k} = 1mA$$

$$I_B = \frac{I_E}{\beta} = 10\mu A$$

$$I_E = 1.01mA$$

$$I_1 = \frac{1.01mA}{10} = 101\mu A$$

$$I_2 = I_1 - I_B = 91\mu A$$

$$R_E = \frac{4.3V}{1.01mA} = 4.26k\Omega$$

$$R_{B1} = \frac{15V - 5V}{101\mu A} = 99k\Omega$$

$$R_{B2} = \frac{5V}{91\mu A} = 54.95k\Omega$$


For the best cost efficiency,  $C_{C2}$  should short first,  $C_{C1}$  should short second,  $C_E$  should short last.

Thus 10/s corresponds to  $C_{C1}$ , 100/s corresponds to  $C_{C2}$ , 1000/s corresponds to  $C_E$ .

$$g_m = \frac{I_E}{V_T} = \frac{1mA}{25mV} = 0.0402$$

$$V_{rc} = \frac{V_o}{g_m} = 2.5kV$$

Low Frequency SS model:

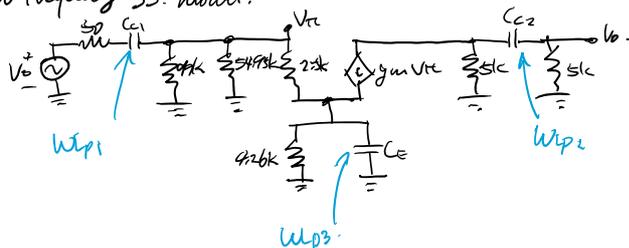

First  $\omega_{LP1} = (C_{C2} \cdot (5k + 5k))^{-1} = 100/s$

$$C_{C2} = \frac{(10)}{10k} = 1\mu F$$

Next, with  $R_E$  open (OCTC test), we have

$$\omega_{LP2} = \left\{ C_{C1} \cdot \left[ 50 + 99k // 54.95k // \left( (1+p)(4.26k) + 2.5k \right) \right] \right\}^{-1} = 10/s$$

$$\Rightarrow C_{C1} \cdot [ \dots ] = 10s$$

$$\Rightarrow C_{C1} = 3.06\mu F$$

Lastly, with all capacitors shorted (SCTC test), we have

$$\tau_{SC}^{CE} = \frac{1}{\omega_{LP3}} = \frac{1}{1000} s = C_E \cdot \left[ \left( (50 // 99k // 54.95k) + 2.5k \right) \left( \frac{1}{1+p} \right) // 4.26k \right]$$

$$\Rightarrow C_E = 39.843\mu F$$