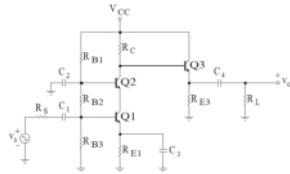


Problem Set 5 (Again)


November 12, 2017 16:26

1. For the circuit in Figure 1, do the following:


- Draw the high-frequency small-signal model.
- Show that $v_{c1} = v_{c2}$ at midband, irrespective of whether $\beta_1 = \beta_2$ or not.
- Find expressions for the 3 high-frequency poles.
- Which of the 3 high-frequency poles do you think will be the dominant pole. Briefly explain your choice.



a. After Miller.

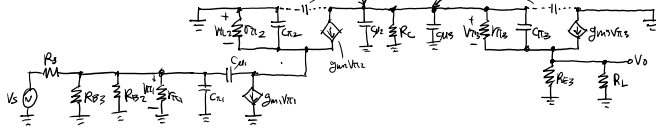


b. Midband:

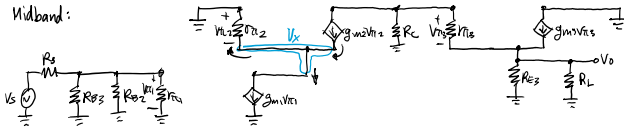

$$\begin{aligned}
 KLL: \quad g_{m2}V_{c2} &= g_{m1}V_{c1} + \frac{V_{c1}}{r_{\pi 2}} \quad g_{m1} = \frac{I_{c1}}{V_T} = \frac{P}{V_T} \quad V_{c1} = -V_{c2} \\
 \frac{I_{c2}}{V_T} \cdot V_{c2} &= \frac{I_{c1}}{V_T} \cdot V_{c1} - \frac{V_{c2}}{r_{\pi 2}} \\
 \frac{I_{c1}}{V_T} \cdot V_{c1} &= \frac{I_{c2}}{V_T} \cdot V_{c2} + \frac{V_{c2}}{r_{\pi 2}} \\
 &= \frac{P}{V_T} \cdot V_{c2} + \frac{V_{c2}}{r_{\pi 2}} \\
 &= V_{c2} \left(\frac{P}{V_T} + \frac{1}{r_{\pi 2}} \right) \quad V_T = \frac{P}{g_{m1}} = \frac{P}{I_{c1}} \\
 &= V_{c2} \left(\frac{P}{V_T} + \frac{1}{r_{\pi 2}} \right) \\
 \frac{I_{c1}}{V_T} \cdot V_{c1} &= V_{c2} \left(\frac{P}{V_T} + \frac{1}{r_{\pi 2}} \right) \cdot I_{c1} \\
 I_{c1} \cdot V_{c1} &= V_{c2} \left(\frac{P}{V_T} + \frac{1}{r_{\pi 2}} \right) \cdot I_{c1} \\
 \cancel{I_{c1}} \cdot V_{c1} &= V_{c2} \cdot \cancel{I_{c1}} \cdot \frac{P}{V_T} + \frac{I_{c1}}{r_{\pi 2}} \cdot V_{c2} \\
 V_{c1} &= V_{c2}
 \end{aligned}$$

c. Between Q1 and Q2, $V_{c1} = V_{c2} = -V_{c2} \rightarrow k = -1$, Miller $C_{M1}' = C_{M1}(1-k)$
 $C_{M1}' = C_{M1}(1-k)$
 $C_{M1}' \approx \frac{C_{M1}}{2}$

Circuit:

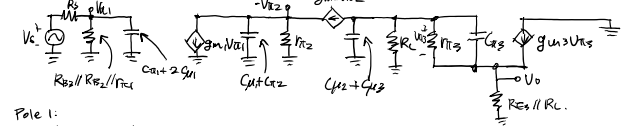

Pole 1:

$$\tau_{p1} = (C_{M1} + 2C_{M1}) \left(R_{B1} \parallel R_{B2} \parallel R_{B3} \parallel r_{\pi 1} \right) < R_B \text{ (small)}$$

Pole 2:

$$\tau_{p2} = (C_{M1} + C_{M2}) \left(r_{\pi 2} \right)$$

Kilohms range

Pole 3:

$$\tau_{p3} = (C_{M2} + C_{M3}) \left(R_{C2} \parallel (r_{\pi 3} + (1+\beta)(R_{E3} \parallel R_L)) \right)$$


Kilohms

d. Pole 2 and 3 are possibly dominant poles
 since $\tau_{\text{nodes}} = \sqrt{C_{M1}^2 + C_{M2}^2 + \dots}$ (Bigger \rightarrow more dominant)

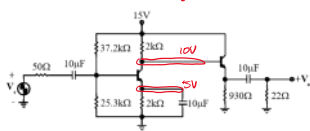2) Give the transfer function of the circuit shown in figure 2 with numerical values for the poles, zeros and midband gain. You may assume that $V_{C1} = V_{B2} = 10V$ and that $V_{B1} = 5V$. You may also assume that the pole and zero associated with C_{C1} cancel one another (essentially C_{C1} doesn't exist)

Default values:

$$\beta = 100, C_C = 10\mu F, C_M = 1\mu F$$



DC:

$$\begin{aligned}
 I_{c1} &= 2.5mA \\
 I_{c2} &= 2.475mA \\
 I_{c1} &= 0.25mA \\
 V_{B1} &= 5.7V \\
 I_{c2} &= 0.225mA
 \end{aligned}$$

$$g_{m1} = \frac{I_{c1}}{V_T} = 0.099W$$


$$r_{\pi 1} = 1.01k\Omega$$

$$I_{c2} = 10\mu A$$

$$I_{c2} = 9.9\mu A$$

$$g_{m2} = \frac{I_{c2}}{V_T} = 0.396$$

$$V_{c2} = 252.5\Omega$$

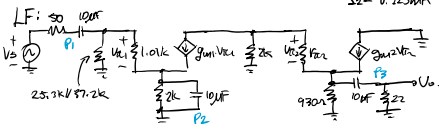

$$\begin{aligned}
 P_3: \quad \omega_{HP3} &= \left[(2k + V_{c2}) \left(\frac{1}{1+\beta} \right) \parallel 2.2 \right] \cdot 10\mu F \\
 &= (192.10\mu F)^{-1} \\
 &= 2285 \text{ rad/s}
 \end{aligned}$$

DC/AC/SC/TC for P1 and P2:

$$\begin{aligned}
 \tau_{c1} &= 10\mu F \cdot 50 + (2.5k \parallel 37.2k \parallel (1+\beta)2k + R_{E1}) \\
 &= 10\mu F \cdot 14.4k \\
 &= 0.144 \text{ s} \leftarrow \text{lower frequency} \\
 \tau_{c2} &= (2.5k \parallel 37.2k + 1.01k) \left(\frac{1}{1+\beta} \right) \parallel 2k \cdot 10\mu F \\
 &= 1.474 \times 10^{-3} \text{ s} \\
 \tau_{c3} &= 10\mu F \cdot (50 \parallel 37.2k \parallel 37.2k) + 1.01k \left(\frac{1}{1+\beta} \right) \parallel 2k \\
 &= 1.044 \times 10^{-3} \text{ s}
 \end{aligned}$$

$$\omega_{P1} = \frac{1}{0.144} = 7.092 \text{ rad/s}$$


$$\omega_{P2} = 9878.3 \text{ rad/s}$$

Zeros:

$$\omega_{Z1} = \omega_{Z2} = 0$$

$$\omega_{Z3} = \frac{1}{2k \cdot 10\mu F} = 50 \text{ rad/s}$$
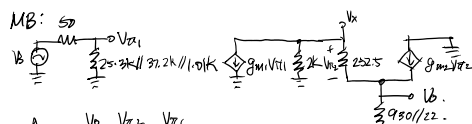
$$F_C(s) = \left(\frac{s}{s + 91.77} \right) \left(\frac{s}{s + 7.092} \right) \left(\frac{s + 50}{s + 9518} \right)$$



$$A_{M1} = \frac{V_{c1}}{V_{c2}} \cdot \frac{V_{c2}}{V_{c1}} \cdot \frac{V_{c1}}{V_{c2}}$$

$$\frac{V_{c1}}{V_{c2}} = \frac{2.5k \parallel 37.2k \parallel (1.01k)}{2.5k \parallel 37.2k \parallel (1.01k + 50)} = 0.75$$

$$V_{c1} = -g_{m1} V_{c1} (2k + 252.5 + (1+\beta)(930/22))$$


$$V_{c1} = -108.47 V_{c1} \rightarrow K = -108.47$$

$$V_{c2} = \frac{V_{c1} \cdot (930/22)}{(930/22) + (1+\beta)(252.5)}$$


$$V_{c2} = 0.996 V_{c1}$$

$$\frac{V_{c2}}{V_{c1}} = -97.168 V_{c1}$$

$$A_{M1} = -97.168 V_{c1}$$

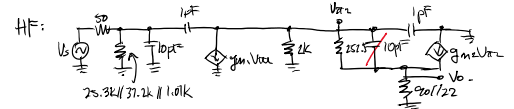
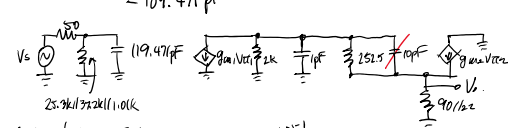
$$\text{Miller: } C_{M1}' = C_{M1}(1-K) = 109.471 \text{ pF}$$





$$\omega_{HP1} = (19.471 \text{ pF} \cdot (50 \parallel 2.5k \parallel 37.2k \parallel 101k))^{-1}$$

$$\omega_{HP2} = (1 \text{ pF} \cdot (2k \parallel 252.5 + (1+\beta)(90/22)))^{-1}$$

$$H_f = \left(\frac{\omega_{HP1}}{s + \omega_{HP1}} \right) \left(\frac{\omega_{HP2}}{s + \omega_{HP2}} \right)$$

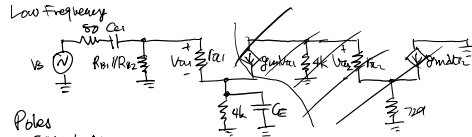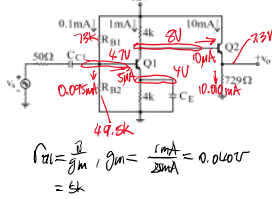3) The designers of the circuit shown in figure 3 have used a 1/3 rule to bias the amplifier shown. They have also used "pole-zero cancellation" to give the amplifier the low frequency amplitude response of a single time-constant circuit and have put ω_{LdB} at 1500/s. Assume that $\beta_1 = 200$ and that $\beta_2 = 1000$. What are the values of C_E and C_{C1} ? ($C_E = 26.6 \mu F$; $C_{C1} = 3.8 \mu F$)



Poles
Sect test:

$$\tau_{C_{C1}} = C_{C1} \cdot (50 + R_{B1} \parallel R_{B2} \parallel R_{C1})$$

$$\tau_{C_E} = C_E \cdot (50 \parallel R_{B1} \parallel R_{B2} + R_{C2} \parallel (1 + \beta_2) \cdot 4k)$$

Oct test:

$$\tau_{C_{C1}} = C_{C1} \cdot (50 + R_{B1} \parallel R_{B2} \parallel (R_{C1} + (1 + \beta_1) \cdot 4k))$$

$$\tau_{C_E} = C_E \cdot (50 \parallel R_{B1} \parallel R_{B2} + R_{C2} \parallel (1 + \beta_2) \cdot 4k)$$

Pole-zero cancellation \Rightarrow a pole and zero share the same location:

Since the only pole $\tau_{C_{C1}} \neq \tau_{C_E}$,
It follows that $\tau_{C_{C1}} = \tau_{C_E}$.

They cancel each other out

Thus leaving us with one pole at $\tau_{C_E} = 1500 \text{ rad/s}$


$$1500 \text{ rad/s} = \frac{1}{\tau_{C_E}}$$

$$\Rightarrow C_E = 26.67 \mu F$$

Since $\tau_{C_{C1}} = \tau_{C_E} = 26.67 \mu F$

$$\Rightarrow C_{C1} = 3.74 \mu F$$

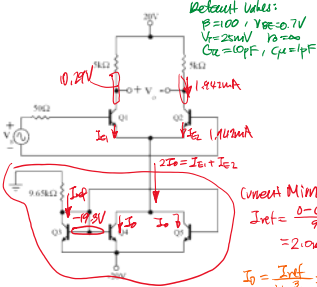4) Assuming that the differential amplifier shown in figure 4 is attached to a load consisting of a $10k \Omega$ resistor in parallel with a 100 pF capacitor, find the value of the β and the high frequency 3 dB point. ($A_{mid} = -196 \text{ V/V}$; $\omega_{HdB} = 1.98 \times 10^5 \text{ rad/s}$)



Design Notes:
 $\beta = 100$, $V_{BE} = 0.7 \text{ V}$
 $V_T = 25 \text{ mV}$, $V_B = 0$
 $C_{C1} = 10 \text{ pF}$, $C_{C2} = 1 \text{ pF}$

Correct Mirror:

$$I_{ref} = \frac{0 - (-19.3 \text{ V})}{9.65 \text{ k}\Omega} = 2.0 \text{ mA}$$

$$I_0 = \frac{I_{ref}}{14 \cdot \frac{2}{\beta}} = \frac{2.0 \text{ mA}}{14 \cdot \frac{2}{100}} = 1.42 \text{ mA}$$

$$2I_0 = 2.84 \text{ mA} = I_{E1} + I_{E2}$$

Assuming Q_1 and Q_2 are identical:

$$I_{E1} = I_{E2} = 1.42 \text{ mA}$$

$$\Rightarrow I_{C1} \approx I_{E1} \approx 1.42 \text{ mA}$$


$$I_{C2} \approx I_{E2} \approx 1.42 \text{ mA}$$

$$V_{C1} = V_{C2} = (20 \text{ V}) - (5 \text{ k}\Omega)(1.42 \text{ mA}) = 10.2 \text{ V}$$

$$g_{m1} = g_{m2} = \frac{I_C}{V_T} = 0.078 \text{ V}$$

$$r_{\pi 1} = r_{\pi 2} = 1257.5 \Omega$$

LF/MB SS:

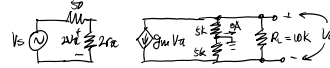


$$2V_s = \left(\frac{2V_s}{2V_s + 50} \right) V_s, \quad V_{C1} = \frac{1}{2} \left(\frac{2V_s}{2V_s + 50} \right) V_s$$

$$V_0 = -g_{m1} V_{C1} \cdot (10 \text{ k}\Omega \parallel 10 \text{ k}\Omega)$$

$$V_0 = (-388.35)(0.470) V_C$$

$$\frac{V_0}{V_s} = A_{mid} = -196.5 \text{ V/V}$$

HF SS:

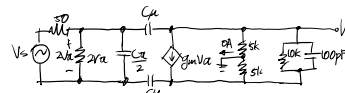

$$\text{Miller: } K = \frac{V_0}{2V_s} = \frac{1}{2} \frac{V_0}{V_s}$$

$$V_0 = -g_{m1} V_{C1} \cdot 5 \text{ k}\Omega$$

$$V_0 = (-388.35)(1) V_C$$

$$\frac{V_0}{V_s} = -388.4$$

$$K = -194.2$$

$$V_0 = \frac{C_{C1}(1-K)}{2} \approx \frac{C_{C1}}{2}$$

$$\tau_{H1} = \left(\frac{C_{C1}}{2} + \frac{C_{C2}}{2} (1-K) \right) (50 \parallel 2V_s)$$

$$= 5.072 \times 10^{-5} \text{ s}$$

$$\tau_{H2} = \left(\frac{C_{C1}}{2} + \frac{C_{C2}}{2} \right) (10 \text{ k}\Omega \parallel 10 \text{ k}\Omega)$$

$$= 5.025 \times 10^{-5} \text{ s}$$

$$\tau_{HdB} = 5.025 \times 10^{-5} \text{ s}$$

$$\omega_{HdB} = 1.99 \text{ Mrad/s}$$