


Problem Set 7 (Again)

November 26, 2017 17:41


Q1. $A=10^4$, $\beta=10^{-2}=0.01$ Actual gain $A_f=7 \times 10^3$

a. $\frac{7 \times 10^3}{10 \times 10^3} = 70\%$ of the intended gain

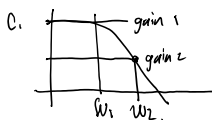
b. $A_f = \frac{A}{1+A\beta}$
 $\frac{dA_f}{dA} = \frac{1}{A} \left(\frac{A}{1+A\beta} \right)'$
 $= \frac{1}{(1+A\beta)^2} + A \cdot \frac{-1}{(1+A\beta)^3} \cdot \beta$
 $= \frac{1}{(1+A\beta)^2} - \frac{A\beta}{(1+A\beta)^3}$
 $= \frac{1+A\beta - A\beta}{(1+A\beta)^3}$
 $= \frac{1}{(1+A\beta)^2}$



Q2. Show that gain = $-R_2/R_1$

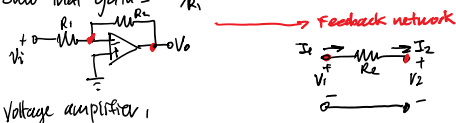

Voltage amplifier,

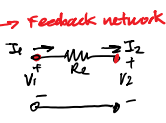


Shunt-shunt topology \rightarrow y-parameters

Recall y-parameters \rightarrow current controlled voltage source

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Recall y-param equivalent circuit:

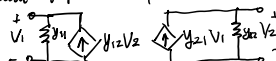



Finding y-parameters:

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{1}{R_2}$$


$$\beta = y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -\frac{1}{R_2}$$

(not important) $y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{1}{R_2}$


$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{1}{R_2}$$

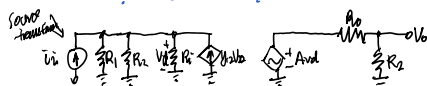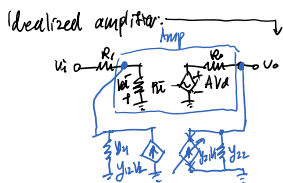

"merge/prune" the sources:

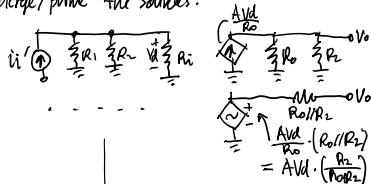

simplifies to

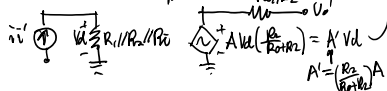

Open loop gain = $\frac{V_o'}{V_i} = \frac{A' \left(\frac{R_1 \parallel R_2 \parallel R_i}{R_1} \right)}{A' \left(\frac{R_1 \parallel R_2 \parallel R_i}{R_1} \right)} = A' \left(\frac{R_1 \parallel R_2 \parallel R_i}{R_1} \right)$
 $A' \left(\frac{R_1 \parallel R_2 \parallel R_i}{R_1} \right) \leftarrow$ open loop gain.

From the idealized amplifier, closed loop gain is $A_f = \frac{V_o}{V_i}$, where $i_i = V_i \cdot R_1$.

$$A_f = \frac{V_o}{V_i} = A' \cdot \frac{V_o}{V_i}$$

But A_f is the gain with units V/V , we want the voltage gain: $\frac{V_o}{V_i}$.


Thus Voltage gain $A_v = \frac{V_o}{V_i}$, $V_i = i_i R_1 \rightarrow A_v = \frac{V_o}{i_i R_1}$

Notice that $A_f = \frac{V_o}{V_i}$, but if the open loop gain A' is large, $A_f = \frac{V_o}{V_i} \rightarrow \frac{1}{\beta}$.

And $\frac{1}{\beta} = \left(\frac{1}{R_2} \right) = -R_2$.

Thus $A_v = \frac{V_o}{V_i R_1} = \frac{A_f}{R_1} = \boxed{-\frac{R_2}{R_1}}$

Q3.


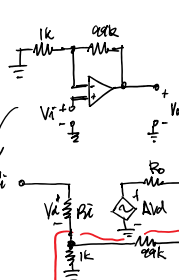


Non-inverting amp: $A=10^5$ V/V , $BW=10$ Hz

Topology: Voltage-series (or series-shunt) \Rightarrow use h-parameters.

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} = 1k \parallel 99k = 990$$

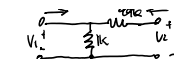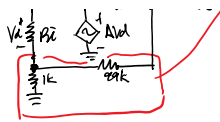

$$u_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} = 1k \parallel 10k = 909 \Omega$$

$$\beta = h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} = \frac{1k}{1k+10k} = 0.0909$$

$$u_{e1} = \frac{I_2}{I_1} \Big|_{V_2=0} = \text{not important}$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} = \frac{1}{10k} = 1 \times 10^{-5}$$

With feedback:

gain:

$$A_f = \frac{A}{1+A\beta} = \frac{10^5}{1+10^5(0.0909)} = 99.9 \%$$

BW: $BW_f = BW(1+A\beta) = 10.01 \text{ kHz}$


If $A = 5 \times 10^4$:

gain:

$$A_f = \frac{A}{1+A\beta} = \frac{5 \times 10^4}{1+5 \times 10^4(0.0909)} = 99.8 \%$$

BW: $BW_f = BW(1+A\beta) = 5.01 \text{ kHz}$

Q4. Find A_{v1} , Z_{i1} , Z_{o1}

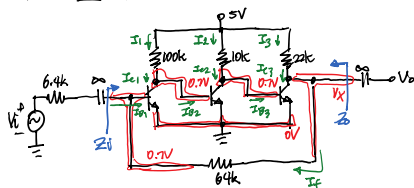

If $V_x > 0.7V$, then $I_3 = \frac{5-V_x}{22k} < \frac{1}{2} \left(\frac{5-0.7}{10k} \right)$

Given default $\beta_{FE} = 100$, it follows that $I_{B3} < 1/2$ of I_{E2} .

Thus we can make the assumption that $I_2 \approx I_{E2}$.

$$\Rightarrow I_{E1} \approx \frac{5-0.7V}{10k} = 430 \mu A$$

$$I_{B1} = 4.3 \mu A$$

$$I_{E1} = I_1 - I_{B1} = \frac{5-0.7}{100k} - 4.3 \mu A = 38.7 \mu A$$

$$I_{B1} = 0.387 \mu A$$

Capacitor decoupling,

$$\Rightarrow I_{B1} = I_f$$

Voltage across 64k: $64k \cdot 0.387 \mu A = 0.0248V$

$$\Rightarrow V_x = 0.7V + \text{voltage across the } 64k = 0.725V$$

Finally calculate missing pieces,

$$\Rightarrow I_3 = I_{E3} = \frac{5-0.725V}{22k} = 194.33 \mu A$$

$$I_{B3} = 1.943 \mu A \quad (\text{Less than } 1/2 \text{ of } I_{E1}, \text{ as expected})$$

Calculating BJT parameters:

$$g_{m1} = \frac{I_{E1}}{V_T} = 0.00155 S$$

$$g_{m2} = 0.0012 S$$

$$g_{m3} = 0.00177 S$$

$$r_{\pi 1} = 64.6k \Omega$$

$$r_{\pi 2} = 5.81k \Omega$$

$$r_{\pi 3} = 12.855k \Omega$$

Redrawing the model at midband (∞ capacitors shorted, DC sources shorted)



Feedback is sampling voltage and gives current to the input, thus the topology is shunt-shunt, use Y-parameters.

Y-parameters:

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{1}{64k}$$

$$y_{21} = \dots$$

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -\frac{1}{64k} = -\beta$$

$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{1}{64k}$$

Simplifying the circuit:




$$V_{x2} = -g_{m1}V_{x1} \cdot (100k \parallel r_{\pi 2})$$

$$= -8.51V_{x1}$$

$$V_{x3} = g_{m2}V_{x2} \cdot (10k \parallel r_{\pi 3})$$


$$= -96.776V_{x2}$$


$$= 823.66V_{x1}$$

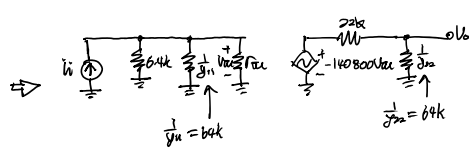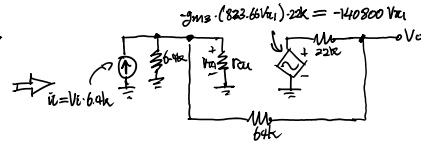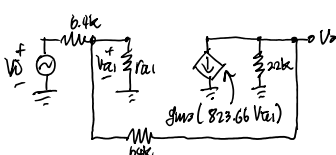

Because of the chosen shunt-shunt topology, which is current controlled voltage source, we make the input a current source, and output a voltage source.

Further simplification:

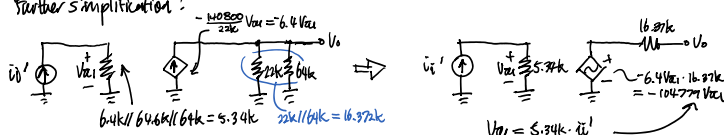

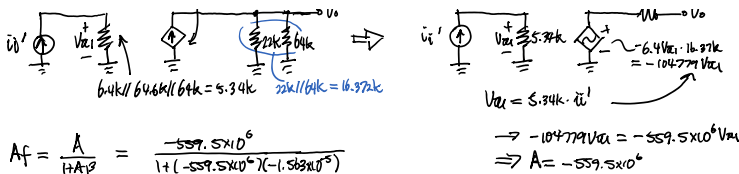

$$A_f = \frac{A}{1+A\beta} = \frac{-559.5 \times 10^6}{1 + (-559.5 \times 10^6)(-1.563 \times 10^{-5})}$$

$\beta = \beta_{12} = -1.563 \times 10^{-5}$
 $A\beta = 8745$

$$A_f = -63.99k\Omega = \frac{V_o}{i_i'}$$

$$A_m = \frac{V_o}{V_i}, \text{ but } V_i = i_i' \cdot 6.4k, A_m = \frac{V_o}{i_i' \cdot 6.4k} = \frac{V_o}{V_i} \cdot \frac{V_i}{i_i' \cdot 6.4k}$$

$\rightarrow A_m = \frac{-63.99k\Omega}{6.4k} = -9.999$

Input Impedance:

$$R_i' = 6.4k \parallel 64.6k \parallel 64k = 5.34k \text{ (with same impedance)}$$

$$R_{if} = R_i' \parallel \frac{1}{A\beta} = 5.34k \parallel \left(\frac{1}{8745} \right) = 0.611\Omega = R_i \parallel 6.4k \text{ (since we want the part w/o source impedance)}$$


$\Rightarrow R_o = 0.611\Omega$

Output Impedance

$$R_o' = 22k \parallel 64k = 16.97k$$

$$R_{of} = \frac{R_o'}{1+A\beta} = \frac{16.97k}{8745} = 1.92\Omega$$

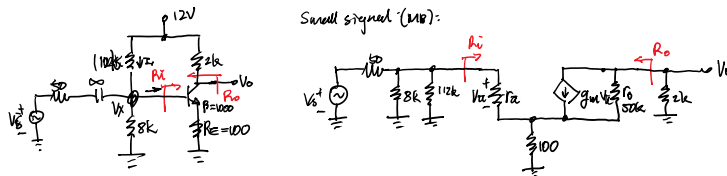Q5. Use series-series topology \rightarrow Z-parameter \rightarrow Voltage controlled current source




DC operating point:

$$\begin{cases} I_2 = \frac{V_x}{12k} = \frac{V_x}{8k} + I_B \\ V_x - 0.7 = (1+\beta)I_B \end{cases} \Rightarrow V_x = 0.793V, I_B = 0.93\mu A$$

$I_E = 0.93mA$
 $\beta_{M1} = 0.037$
 $r_E = 26.89k\Omega$

Feedback Network:

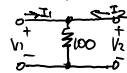

Z-parameters:


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = 100$$


$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = 100 = \beta$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = 100$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = 100$$

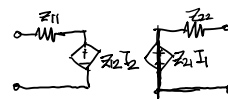

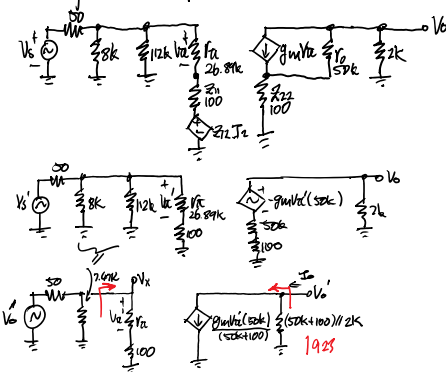Small signal with Z-param equivalent circuit:



$$A_v = \frac{V_o}{V_s}$$

$$V_o = g_m V_{GS} \left(\frac{52k}{30k+100} \right) \left(\frac{50k+100}{2k} \right)$$

$= -71.401 V_{GS}$
 $V_{GS}' = V_x \left(\frac{100}{100+12k} \right) = 0.004 V_x$

$$V_o = -0.265 V_x$$

$$V_x = \frac{(12k+100) \parallel 2.47k}{(12k+100) \parallel 2.47k + 50} V_s$$

$$= 0.992 V_s$$


$$V_o = -0.262 V_s$$

$$A_v = \frac{V_o}{V_s} = -0.262$$

Q6. A TF: $T(s) = \frac{10^4}{(1 + \frac{s}{10^3})(1 + \frac{s}{10^5})} = \frac{10^4 \cdot 10^6 \cdot 10^8}{(s+10^3)(s+10^5)(s+10^8)} = \frac{10^{18}}{(s+10^3)(s+10^5)(s+10^8)}$

Bode Plot:

$$|T(j\omega)| = 20 \log_{10}(10^4) = 80 \text{ dB}$$

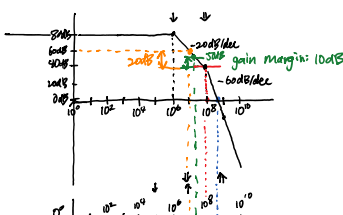


b) want P such that ph-margin = 45°
(angle = -135°)

at the frequency at which $\theta = -135^\circ$,
magnitude is 50 dB,

$$\Rightarrow 20 \log_{10}\left(\frac{1}{P}\right) = 50 \text{ dB}$$

$$P = 3.162 \times 10^{-3}$$

c). 10 dB

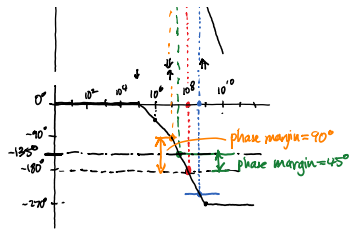

$$\Rightarrow 20 \log\left(\frac{1}{\beta}\right) = 50 \text{ dB}$$

$$\beta = 3.16 \times 10^{-3}$$


c). 10 dB

d). $20 \log\left(\frac{1}{\beta}\right) = 40 \text{ dB}$, $\beta = \frac{1}{10^2} = 0.01$

e). when $\beta = 10^{-3}$, $20 \log\left(\frac{1}{\beta}\right) = 60 \text{ dB}$
 gain margin = 20 dB
 phase margin = 90°


Q7.

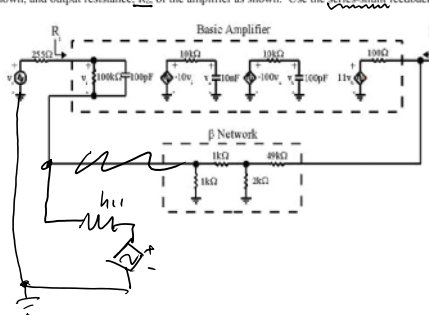7. For the circuit shown in figure 5 use feedback techniques to find the mid band gain, $A_M = v_o/v_i$, the gain margin, G.M., the phase margin, P.M., $\phi_p = \phi_u - \phi_m$, the input resistance, R_i , of the amplifier as shown, and output resistance, R_o , of the amplifier as shown. Use the series-shunt feedback topology.



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Feedback Network:

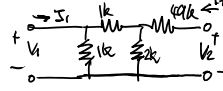


$$h_{11} = \frac{V_1}{I_1} \bigg|_{V_2=0} = \left(\frac{49k \parallel 2k \parallel 1k}{1k} \right) = 745 \Omega$$

$$h_{12} = \frac{V_1}{V_2} \bigg|_{I_1=0} = \left(\frac{1k}{1k \parallel 49k} \right) \cdot 0.5 = 0.010 \text{ V/V}$$


h_{21} = don't care

$$h_{22} = \frac{I_2}{V_2} \bigg|_{I_1=0} = \frac{1}{(2k \parallel 12k) \parallel 149k} = \frac{1}{5k} = 2 \times 10^{-5} \text{ S}$$

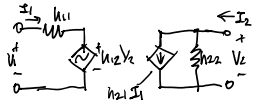Equivalent circuit of the feedback network



Ideal Amplifier:

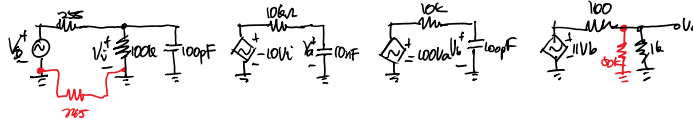

Embedding everything: $V_s \rightarrow V_s'$, $V_o \rightarrow V_o'$

$$A_M' = \frac{V_o'}{V_i'} = \frac{V_o'}{V_o} \cdot \frac{V_o}{V_a} \cdot \frac{V_a}{V_i'} = \frac{V_o'}{V_o} \cdot \frac{V_o}{V_a} \cdot \frac{V_i'}{V_s}$$

$$\frac{V_o'}{V_o} = 11 \cdot \left(\frac{980}{980 \times 100} \right) = 9.982$$

$$\frac{V_o}{V_a} = -100 \text{ (high-freq capacitor acts open)}$$

$$\frac{V_a}{V_i'} = -10 \text{ (high-freq capacitor acts open)}$$

$$\frac{V_i'}{V_s} = \frac{100k}{100k + 255 + 745} = 0.19$$

$$A_M' = 9883.02 \text{ V/V}$$

$$R_i = 255 + 745 + 100k = 101k$$

$$R_{if} = R_o (1 + A\beta)$$

$$R_{in} = R_{if} - 255$$


$$\text{Feedback Gain: } A_f = \frac{A'}{1 + A'\beta} = \frac{9883}{1 + 9883(0.01)} = 98.978 \text{ V/V}$$

For Bode plots, need to find pole locations:

$$\omega_{p1} = \frac{1}{10k \cdot 100pF} = 10^3 \text{ rad/s}$$

$$\omega_{p2} = \frac{1}{10k \cdot 10nF} = 10^4 \text{ rad/s}$$
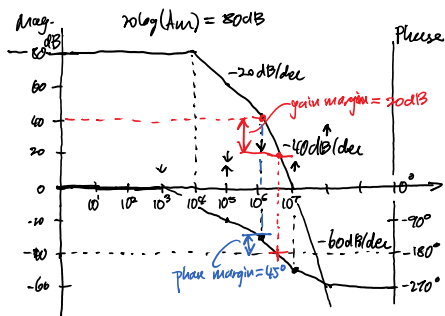
$$\omega_{p3} = \frac{1}{10k \cdot 100pF} = 10^6 \text{ rad/s}$$



$$20 \log\left(\frac{1}{\beta}\right) = 40 \text{ dB}$$

$$R_{of} = \frac{50k \parallel 1k \parallel 100}{1 + A\beta} = 10k$$