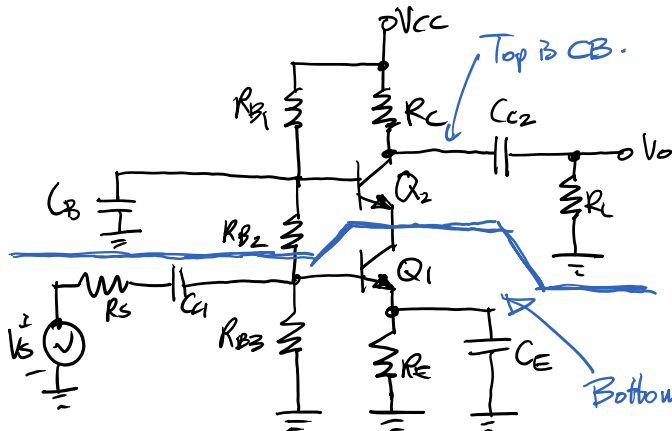


The Cascode

October 24, 2017 3:34 PM



Problem with common emitter:


Miller effect \rightarrow Big capacitance
 \rightarrow limited bandwidth

Problem with common base:

small input impedance \rightarrow small gain.

Usually C_B & C_E is very large. (since this model is very hard to analyze impedance)

Midband Small Signal Model

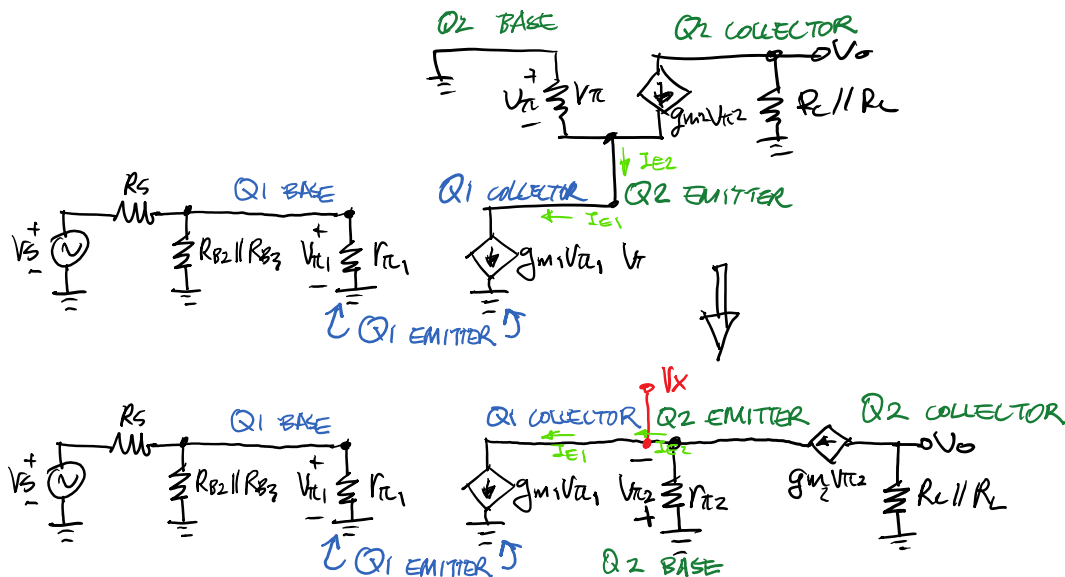

$$g_{m1}V_{\pi 1} = g_{m2}V_{\pi 2} + \frac{V_{\pi 2}}{r_{\pi 2}}$$

$$\frac{I_{c1}}{V_T}V_{\pi 1} = \frac{I_{c2}}{V_T}V_{\pi 2} + \frac{V_{\pi 2}}{r_{\pi 2}} \quad g_{m2} = \frac{I_{c2}}{V_T} = \frac{\beta_2}{r_{\pi 2}}$$

$$= \left(\frac{\beta_2 + 1}{r_{\pi 2}} \right) V_{\pi 2}$$

$$= \left(\frac{\beta_2 + 1}{\beta_2} \right) \frac{I_{c2}}{V_T} V_{\pi 2}$$

$$I_{c1}V_{\pi 1} = \left(\frac{\beta_2 + 1}{\beta_2} \right) I_{c2}V_{\pi 2}$$

$$I_{c1}V_{\pi 1} = I_{c2}V_{\pi 2}$$

$I_{c1} = I_{c2}$ (emitter of Q2 is connected to collector of Q1)

$$\rightarrow V_{\pi 1} = V_{\pi 2}$$

$$\rightarrow V_x = -V_{\pi 1} = -V_{\pi 2}$$

$$\rightarrow V_{\pi 1} = V_{\pi 2}$$

$$\rightarrow V_x = -V_{\pi 1} = -V_{\pi 2}$$

↑
Needed for Miller Theorem


$$A_{m1} = \frac{V_o}{V_{\pi 2}} \cdot \frac{V_{\pi 2}}{V_{\pi 1}} \cdot \frac{V_{\pi 1}}{V_s}, \quad \frac{V_{\pi 2}}{V_{\pi 1}} = 1$$

$$= \frac{V_o}{V_{\pi 2}} \cdot \frac{V_{\pi 1}}{V_s}$$


$$= -\cancel{g_{m2} V_{\pi 2}} \times R_c \parallel R_L \cdot \left(\frac{\cancel{V_s} \cdot R_{B2} \parallel R_{B3} \parallel r_{\pi 1}}{R_s + R_{B2} \parallel R_{B3} \parallel r_{\pi 1}} \right)$$

$$= -g_{m2} (R_c \parallel R_L) \cdot \frac{R_{B2} \parallel R_{B3} \parallel r_{\pi 1}}{R_s + R_{B2} \parallel R_{B3} \parallel r_{\pi 1}}$$

High Frequency

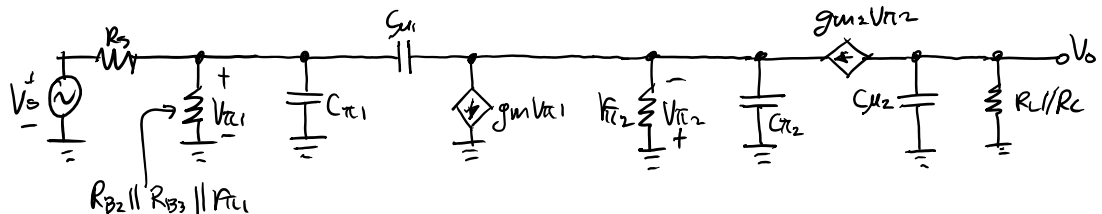

MILLER:

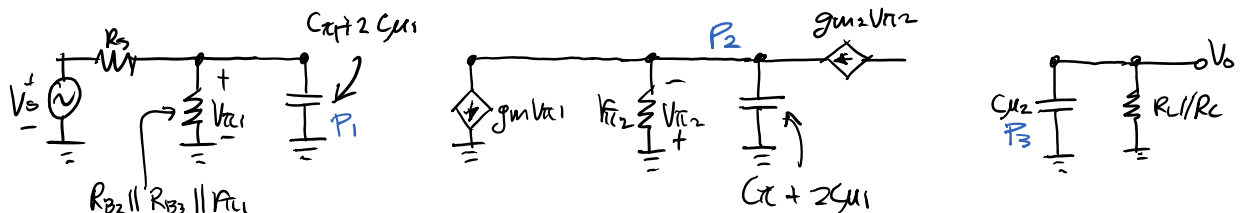

$$\omega_{HP1} = \frac{1}{(C_{\pi 1} + 2C_{\mu 1})(R_s \parallel R_{B2} \parallel R_{B3} \parallel r_{\pi 1})}$$

$$\omega_{HP2} = \frac{1}{\left(\frac{r_{\pi 2}}{1 + \beta_2} \right) (C_{\pi 2} + 2C_{\mu 1})}$$

$$\omega_{HP3} = \frac{1}{(C_{\mu 2})(R_L \parallel R_c)} \quad \leftarrow \text{possible dominant pole.}$$

Biasing Cascode

